


amateur radio

Vol. 37, No. 3

MARCH, 1969

Registered at G.P.O., Melbourne, for
transmission by post as a periodical

PRICE 30 CENTS

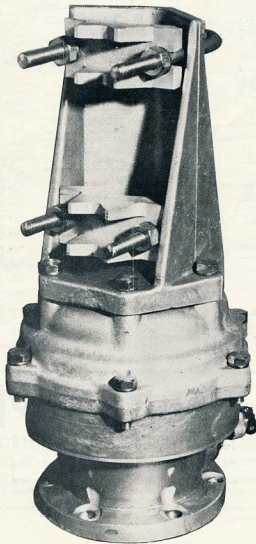

CLEAR PLASTIC PANEL METERS

MR1P 1 1/4 inch square, clear plastic, 1 inch round mounting hole, 1 1/4 inch deep:

1 milliamperes (mA.) \$3.50
100 microamperes (uA.) \$3.75
5 amperes (A.) \$4.75
Also other types available.

MR2P 1 1/4 inch square, clear plastic face, 1 1/4 inch round mounting hole, 1 1/4 inch deep:

50 uA. \$5.50 1-0.1 mA. \$4.00
50-50 uA. \$5.75 1, 5, 10 A. \$3.75
100 uA. \$5.40 15, 30 A. \$3.75
100-0-100 uA. \$5.50 15 volt d.c. \$3.75
500 uA. \$4.50 30 volt d.c. \$3.75
1 mA. \$3.75 300 volt a.c. \$4.25
5, 10, 25, 50, 100, 250, 500 mA. \$3.75 1000 volt a.c. \$4.50

"S" Meter (1 mA. f.s.d.) cal. 0-9 (with additional scale in 10 db. steps over 99) \$5.25

"VU" Meter, scale: minus 20 to plus 3 VU (0 to plus 3 VU in bold red arc). Accuracy: within plus or minus 0.5 db. (at 0 VU) \$5.00

Stereo Balance Meter (1-0-1 mA. f.s.d.) \$4.50
Also other types available.

MR3P 3/4 inch square, clear plastic face, 2 1/4 inch round mounting hole, 1 1/4 inch deep:

50 uA. \$7.00 50-0-50 uA. \$5.75
100 uA. \$6.75 15 volts d.c. \$5.75
500 uA. \$6.50 25 volts d.c. \$5.75
1, 5, 10, 25, 50 300 volts a.c. \$5.75
100, 250, and "VU" Meter \$8.25
500 mA. \$5.75

P25 2 1/4 inch square, clear plastic face, 2 1/4 inch mounting hole, 1 1/4 inch deep:

50 uA. \$5.75 15 volts d.c. \$5.50
100 uA. \$5.75 25 volts d.c. \$5.50
500 uA. \$5.25 300 volts a.c. \$5.50
1, 5, 10, 20, 50 "S" Meter \$5.75
250, and 500 "VU" Meter \$5.50
mA. \$5.00
Postage 25c

1 Mc. CRYSTALS

Mounted in octal plug, suitable for BC221 Frequency Meter. To clear. \$8.00.

MINI-TESTER, MODEL C1000

Ranges—AC voltage (1000 ohms/volt): 10, 50, 250, 1000 DC voltage (1000 ohms/volt): 10, 50, 250, 1000 DC current: 1, 100 mA. Resistance: 0-150K ohms. Dimensions: 2 1/4 x 3-9/16 x 1-1/16. Weight 0.37 lb. Price \$6.35, plus postage 20c.

CO-AXIAL CABLE

72 ohms, 100 yds. roll, \$18.00. Postage 75c.

FIVE-CORE CABLE

5 x 5/076. Ideal for Intercoms., Telephones, etc. New. 100 yd. rolls, \$17 (postage 75c), or 20c yd.

DISC CERAMIC CONDENSERS

30 assorted in packs, \$1.20. Postage 10c.

1967 CALL BOOKS

Old stock. Price 45c.

DISPOSALS SPECIALS

TV Tuners, M.S.P., incremental, brand new, complete with valves 6E58 and 6B8. Price \$5.50.

Carbon Resistors. 100 assorted 1/4 and 1 watt. Good selection. All popular types. \$1.75 packet.

Mica Washers and Grommets. 25c packet.

Audio Transformers (A. & R. Type):

10 watts. Primary: 8,000 c.t., ultra linear, 42 p.c. taps. Secondary: 2, 8, 16 ohms. Price \$7.50.

40 watts. Primary: 6800/4500 ohms, push pull. Secondary: 500, 250, 125, 50 ohms. Price \$10.

15 watts. Primary: 10,000/6,000 ohms push pull. Secondary: 2, 4, 8, 15 ohms. Price \$5.50.

5 watts. Primary: 10,000 ohms, single ended. Secondary: 2, 3.5, 8, 15 ohms. Price \$4.00.

Recording Tape Specials. Unboxed Scotch brand. New, guaranteed.

2 Reels, 900 ft., 5 inch. Polyester base, \$3.95. 2 Reels, 1800 ft., 7 inch. Polyester base, \$7.75.

Transistor Driver Transformers. Type AMT-200. Primary imped.: 500 ohms; secondary imped.: 1500 ohms X2. 75c or three for \$2.

ALARM BELLS

(Parachute type). 6 volt. Suitable for Burglar Alarms, etc., complete with trip rope, etc. Price \$1.25, post 50c.

HIGH IMPEDANCE HEADPHONES

New. Price \$2.50. Postage 20c.

LOW IMPEDANCE HEADPHONES

8 ohms. Price \$2.50. Postage 20c.

POCKET RADIO

Type ER22. Complete with ear piece. Price \$1.75. Postage 10c.

TRANSISTOR INTERCOM UNITS

Four-Station: 1 master, 3 sub-stations. Three Transistors. 250 mW. Amplifier. Battery operated (Eveready 216), complete with battery, wire, stations and fitting instructions. Price \$19.75.

Two Station Model also available. Price \$10.50.

Three-Station Intercoms, as per above, one master and two sub-stations. Price \$14.75.

NEW VALVES

1R5	\$1.42	plus tax	6BL5	\$1.19	plus tax
1S2	\$1.14	6BM6	\$1.24
1S4	\$2.22	6BR5	\$1.12
1S5	\$1.35	6BW6	\$1.42
3S4	\$1.35	6CXTOT	\$2.22
3V4	\$1.35	6CM5	\$1.65
5A54	\$1.05	6CW5	\$1.08
5Y3GT	\$2.00	6CW7	\$1.22
6AD5	\$1.08	6CXA	\$1.65
6AE8	\$2.88	6GW8	\$1.31
6AL3	\$1.18	6L6	\$3.52
6AN7	\$1.22	6M5	\$1.04
6AN8	\$1.89	6N3	88c
6AO5	\$1.03	6R3	\$1.18
6AR5	\$1.68	6S2	\$1.42
6ARTGT	\$1.44	6SC7	\$1.86
6AL1GT	\$1.18	6V6GT	\$1.35
6AU6	\$1.05	6X4	75c
6AV6	90c	6Y6	\$1.50
6BA6	\$1.08	9UB	\$1.50
6BD7	88c	12AU7A	\$1.12
6BE6	\$1.09	12AX7	\$1.25
6BH5	\$1.05	80	\$1.15

All above Valves plus 25% Sales Tax

CLARION AUTO RADIO

Model CR208E. New. Push-button tuning superhet. with r.f. amplifier. Tuning range, 530 to 1605 Kc. I.F., 452.5 Kc. Sensitivity, less than 20 db. Selectivity, more than 20 db. at plus or minus 10 Kc. Output, more than 3.5w. 6 transistors and 3 diodes. Power supply, 6v. DC negative ground, less than 1.2A. 12v. DC negative or positive ground, less than 0.8A. Price \$59.50. Postage 70c.

HI-INTENSITY LAMP

240 volt input to 12 volt globe. (Built-in transformer.) Arm swivel in any position. Price \$3.75. Postage 20c.

AUTO CAR AERIALS

Hirschmann, type 300M, slide mounting, new. Price \$4.50. Postage 20c.

SIGNAL INJECTOR

Model SE2508. Price \$7.00. Postage 20c.

CRYSTAL MICROPHONES

Price only

\$5.50

Stand to suit

\$2.50 extra.

Packing and Postage 25c.

Model BM3 (Illustrated): Response 100-8,000 cycles, fitted with 6 ft. cable and phone plug with on-off switch. Can be used on stand or for hand use. BM3 insert, \$1.00 each

PANEL METERS

Brand New in Cartons. Plus Postage 20c

Type F307: 0-50 uA., 2 1/4 in. round, mounting hole 1 1/16 in. Price \$3.75.

Type F351: 0-200 uA., 2 1/4 in. square, mounting hole 1 1/4 in. Price \$3.75.

Type F386: 500-0-500 uA., 2 1/4 in. square, mounting hole 1 1/4 in. Price \$3.50.

0-10 volts AC, 3 in. square, mounting hole 2 1/4 in. Price \$4.00.

Type F471: 50 volts DC, 3 in. square, mounting hole 2 1/4 in. Price \$4.00.

Type F516: 300 volts AC, 2 1/4 in. square, mounting hole 1 1/4 in. Price \$4.00.

Type Q515: 150 volts AC, 2 1/4 in. square, mounting hole 1 1/4 in. Price \$3.50.

Type S045: 20 volts AC, 2 in. square, mounting hole 1 1/4 in. Price \$3.50.

Type F487: 1-0-1 mA., blank scale, 2 1/4 in. square, mounting hole 1 1/4 in. Price \$3.75.

Type F498: 1-0-1 mA., blank scale, 3 1/4 in. square, mounting hole 2 1/4 in. Price \$3.75.

Type F499: 1-0-1 mA., blank scale, 4 1/4 in. square, mounting hole 3 1/4 in. Price \$4.25.

Type F555: 10 mA., blank scale, 2 1/4 in. square, mounting hole 1 1/4 in. Price \$3.00.

Type F498: 50-0-50 uA., blank scale, 2 1/4 in. square, mounting hole 1 1/4 in. Price \$4.00.

Type F491: 50-0-50 uA., blank scale, 3 in. square, mounting hole 2 1/4 in. Price \$4.50.

CURRENT 1969

CALL BOOKS AND LOG BOOKS

Price 75c each.

HAM

RADIO SUPPLIERS

323 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones: 67-7329, 67-4286 All Mail to be addressed to above address

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio Valves and Transistor Radios, Kew Brand Meters, A. & R. Transformers and Transistor Power Supplies, Ducon Condensers, Welwyn Resistors, etc

amateur radio

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA FOUNDED 1910



MARCH 1969
Vol. 37, No. 3

Publishers:

VICTORIAN DIVISION W.I.A.
Reg. Office: 478 Victoria Parade, East Melbourne, Vic., 3002.

Editor:

K. E. PINCOTT VK3AFJ

Assistant Editor:

E. C. Manifold VK3EM

Publications Committee:

G. W. Baly (Secretary) VK3AOM
A. W. Chandler (Circulation) VK3LC
Ken Gillespie VK3GK
M. Tarrant VK3LF

Draftsmen:

Clem Allan VK3ZIV
Peter Ramsay VK3ZWN
Ian Smith 36 Green St., Noble Park

Enquiries:

Mrs. BELLAIRS, Phone 41-3335, 478 Victoria Parade, East Melbourne, Vic., 3002. Hours: 10 a.m. to 3 p.m. only.

Advertising Representatives:

AUSTRALIAN MEDIASERV
21 Smith St., Fitzroy, Vic., 3065. Tel. 41-4952.
P.O. Box 106, Fitzroy, Vic., 3065.

Advertisement material should be sent direct to the printers by the first of each month.

Advertisements should be addressed to the Editor.

Printers:

"RICHMOND CHRONICLE," Phone 42-2419.
Shakespeare Street, Richmond, Vic., 3121.



All matters pertaining to "A.R." other than advertising and subscriptions, should be addressed to:

THE EDITOR,
"AMATEUR RADIO,"
P.O. BOX 38,
EAST MELBOURNE, VIC., 3002.



Members of the W.I.A. should refer all enquiries regarding delivery of "A.R." direct to their Divisional Secretary and not to "A.R." direct. Non-members of the W.I.A. should write to the Victorian Division, C/o. P.O. Box 38, East Melbourne. Two months' notice is required before a change of mailing address can be effected. Readers should note that any change in the address of their transmitting station must, by P.M.G. regulation, be notified to the P.M.G. in the State of residence; in addition, "A.R." should also be notified. A convenient form is provided in the "Call Book".



Direct subscription rate is \$3.60 a year, post paid, in advance. Single copies 30c. Issued monthly on first of the month. February edition excepted.

CONTENTS

Technical Articles:—	Page
An Experimental 455 Kc. I.F. Strip	5
Project—Solid State Transceiver, Part Five	8
The W5OMX Communications Receiver	11
 General:—	
Book Review:	
Electronic Circuit Design Handbook	6
Ham Radio Projects	6
Radio Communications Handbook	6
104 Easy Transistor Projects You Can Build	6
Correspondence	19
"CQ" SSB Award Rules	19
DX	20
Federal Awards	17
Federal Comment	4
Federal Notes	21
New Call Signs	18
New Equipment:	
Log Periodic for 6-2 Metres	17
Motorised Antenna Rotator	17
Panoramic Display Unit	17
Versatile AC Bridge	17
Prediction Charts for March 1969	16
Silent Key	21
The Questionnaire—Some Further Progress	7
VHF	20
W.I.C.E.N. Exercise by VK3 North-Western Zone	17
 Contests:—	
Contest Calendar	19
"CQ" World Wide WPX SSB Contest, 1969	19
1969 I.A.R.C. Propagation Research Competition	19

COVER STORY

Antennas are increasingly in the news these days and our front cover this month shows the working end of a new rotator from Bail Electronic Services. Development of these devices has been such that models like the "Emotator" 1100M, designed with push-button control, are within the economic range of most Amateur uses.

GELOSO AMATEUR-BAND TRANSMITTER

Model G4/225

A complete Transmitter that gives an Amateur all the facilities for modern communications for CW, SSB, DSB, and AM modes.

FEATURING—

- ★ Crystal stabilised VFO.
- ★ 160-200 watts PEP on SSB.
- ★ 80 metres through to 10 metres.
- ★ 16 tubes with a pair of 6146s in PA.
- ★ 100% AM modulation.
- ★ Break-in keying for CW.
- ★ VOX operation.
- ★ Netting switch.
- ★ PI coupler output.
- ★ Modulation meter incorporated.



GELOSO Transmitters, Receivers and VFOs have been marketed in Australia for over 15 years with complete success.

A companion Receiver to the G4/225 is the G4/216. Both are available from stock.

Available direct
from Australian
Agents:

R.H. Cunningham
PTY. LTD.

Send for Technical Bulletin No. 96 for complete information and details.


HAM PRICE: G4/225 Transmitter, \$310.00 plus sales tax.
G4/226 Power Supply, \$124.50 plus sales tax.

608 COLLINS STREET, MELBOURNE, VIC., 3000
Telephone 61-2464

64 ALFRED ST., MILSONS POINT, N.S.W., 2061
Telephone 929-8066

HY-GAIN AMATEUR ANTENNAS

Fully Imported
from U.S.A.

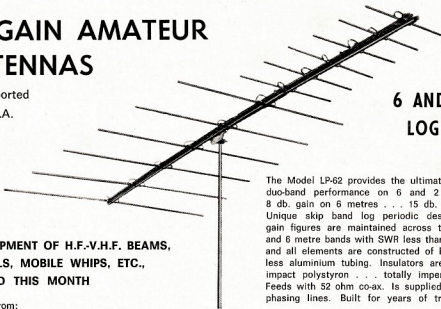

NEW SHIPMENT OF H.F.-V.H.F. BEAMS,
VERTICALS, MOBILE WHIPS, ETC.,
EXPECTED THIS MONTH

Available from:

BAIL ELECTRONIC SERVICES, 60 Shannon St., Box Hill North, Vic., 3129. Ph. 89-2213

Rep. in N.S.W.: A. J. ("SANDY") BRUCESMITH, 47 Hyman Street, Tamworth, N.S.W., 2340. Telephone (STD 067) 66-1010

HY-GAIN'S
6 AND 2 METRE
LOG PERIODIC
MODEL LP-62

The Model LP-62 provides the ultimate in uni-directional duo-band performance on 6 and 2 metres. Delivers 8 db. gain on 6 metres . . . 15 db. gain on 2 metres. Unique skip band log periodic design insures rated gain figures are maintained across the entire 2 metre and 6 metre bands with SWR less than 2:1. Double boom and all elements are constructed of heavy gauge seamless aluminium tubing. Insulators are moulded of high impact polystyrene . . . totally impervious to weather. Feeds with 52 ohm co-ax. Is supplied complete with all phasing lines. Built for years of trouble-free service.

a complete amateur radio station



in one portable package



SWAN Cygnet

A 5-BAND 260 WATT SSB TRANSCEIVER WITH BUILT-IN AC AND DC SUPPLY AND LOUDSPEAKER – \$464 plus tax

The new Swan Cygnet is a complete SSB Transceiver, with self contained AC and DC power supply, microphone and loudspeaker in one portable package. The Cygnet features full frequency coverage of the 10, 15, 20, 40 and 80 metre bands with a power input rating of 260 watts PEP in single sideband mode, and 180 watts CW input. A crystal lattice filter at 5500 Kc. is used in both transmit and receive mode, and provides excellent selectivity with a 2.7 Kc. bandwidth at 6 db. down. Superior receiver sensitivity of better than $\frac{1}{2}$ microvolt makes it easy to pull in those DX signals, and with the Cygnet, if you can hear them, you can work them. Audio fidelity is in the well known Swan tradition of being second to none; providing smooth, natural sounding voice quality. The Cygnet is temperature compensated on all bands, featuring solid state oscillator circuitry with zener regulation which permits wide variation in supply line voltage without frequency shift.

Unwanted sideband suppression is 45 db., carrier suppression 60 db., and distortion products are down approximately 30 db.

The new Cygnet is designed to provide efficient, high quality communications in the five most commonly used Amateur bands. Its low cost is a tribute to Swan's well known techniques in value analysis, and simple, direct circuit design. Above all, these techniques lead to a high degree of reliability and foolproof performance. Dimensions are: 13" wide, 5½" high, and 11" deep. Weight is 24 lbs.

The transceiver comes complete with AC and DC input cords, and carrying handle; thus making it the most versatile and portable set on the market, and certainly the best possible value.

Amateur net \$464 plus Tax

W.F.S. ELECTRONICS SUPPLY CO.

227 VICTORIA ROAD, RYDALMERE, N.S.W., 2116. Phones: 638-1715, 638-1355

SWAN ELECTRONIC SERVICE CO., 14 Glebe Street, Edgecliff, N.S.W., 2027. Phone 32-5465

FEDERAL COMMENT

About 1,000 copies of this issue of "A.R." are being sent out as complimentary copies — perhaps you, the reader are one of these 1,000. This came about because a few months ago the Magazine Committee decided to include a Questionnaire soliciting information about the magazine and Amateur Radio generally; they also asked "Is there anyone to whom you would like a complimentary copy sent?" They were overwhelmed with replies and now have a tiger by the tail!

We hope you find favour with this "house journal" of the Wireless Institute of Australia.

If you are an advertiser you may be interested in the circulation. This magazine reaches nearly 5,000 Amateur Radio operators or people with an associated interest in radio. These are radio "hobbyists," but they are also consumers of many non-related products, and in an estimated 38% of cases they are in positions of responsibility in the electronics industry, or telecommunications, or other related occupations. They are united through their hobby, not through being similarly employed, therefore this journal is, we believe, a unique medium for reaching a diverse group of consumers. In the U.S.A. an estimated 49% of Amateurs are engaged in radio communication, and other electronic and electrical engineering, according to the Stanford Research Institute report of 1967.

So, we suggest, you may care to use our W.I.A. journal to bring before our members information about your products. The support of advertisers is necessary for this journal's continued survival and conversely the supporting of our advertisers is a must as far as we, the Amateurs, are concerned. We should show preference in our purchasing for products regularly advertised in our journal.

If, however, you are not an advertiser, but a non-member Amateur Radio operator who has received this copy as a result of a friend's request for a complimentary copy to be sent to you, then what's in it for you?

Firstly, we hope the editorial material (the technical articles, the notes of Amateur Radio activities, etc.) is of interest to you; secondly, we hope you consider the work being done by Australia's Amateur Society, the W.I.A., is appreciated by you as shown by your support and membership. Two things then are to your benefit—the receipt of a well-produced magazine, and the maintenance of your hobby, through your support of its Society.

Should you merely wish to receive the magazine, then twelve copies at 30 cents each is \$3.60, direct subscription. However, you can receive the magazine at a lower cost per copy—at present 17 cents, but this will cost you a bit more than \$3.60! How's that again? Put it this way, subscriptions to the W.I.A. vary from State to State, and vary from

grade to grade, and range for full members (licensed operators) from \$8.00 in Victoria to about \$5.00 in some other States, but all are considerably above the \$3.60 for 12 copies of "A.R." Why pay more to receive the magazine?

Because, I believe, if you can see your way clear to be a member of the W.I.A. rather than just a direct subscriber to its journal, you give support to its efforts to "represent the Amateur Service". You also support the activities of a large band of enthusiastic honorary officers. (W.I.A. has no fully-paid officers, and honoraria are rare. The editing and production of this magazine are done by voluntary labour, the major costs being paper, printing and postage. Its cost to members is 17 cents a copy.)

Where do the extra few dollars go? How is this W.I.A. organised? There are six States or Divisions, each autonomous, and you pay your sub. to your "Division". Each Division, irrespective of size, carries one vote at the annual Federal Convention where Federal policy is determined. One Division (Victoria), in addition to running its own Divisional affairs, provides the personnel for an independent Federal Executive body to implement decisions of Federal Council. The Victorian Division, in addition, assumes responsibility for publishing this magazine on behalf of the Federal body.

Say for argument that your sub. is \$6.00 p.a. Of this, 17 cents $\times 12 = \$2.04$, goes to the publishers of "A.R." magazine; also about \$1.00 goes to Federal Executive of W.I.A. So about \$3.00 of your say, \$6.00 is remitted from your Division's funds, the remainder is retained in your State for its administration. The \$1.00 to F.E. is made up as follows: 30 cents per member is the annual "per capita" fee, 20 cents per member will be recovered starting this year so that Australia can pay its dues to the Region III organisation of South-East Asian and Oceanic Amateur Radio Societies. The other 50 cents odd (it's been about 47 cents per member on the average over recent years) is used by Federal Council through Executive to finance the annual meeting of delegates from the six Divisions.

The mechanism of this "50 cents odd" calculation is that air fares, accommodation and meals over the Easter period for six delegates and three members of Executive, are placed in an account, stirred around, and the total is divided up between States according to membership. All members of the W.I.A. contribute the same to the cost of the Convention, but the total paid by larger Divisions is, of course, greater. The effect of this procedure is that the travel costs of delegates from States far from the Convention venue are subsidised by States close to the venue. As the Convention is held in rotation around the States, this to a degree evens out over

the years. (This year the Convention is in Canberra, next year it is expected to be in Perth.) However, all W.I.A. members pay the same per capita fee of 30 cents, they pay the same Region III contribution of 20 cents, they pay the same share of Convention costs of about 50 cents, they pay the same price for "A.R." of 17 cents $\times 12 = \$2.04$. So the cost of "Federal" activities and administration is the same for all members, about \$3.00, irrespective of where they reside. The difference between \$3.00 and your actual sub. is the cost of maintaining your State W.I.A. organisation and paying for its administration.

You may care to contact your Divisional Secretary and enquire about membership and subscription, or you may care to send the application form published as an insert to this issue. But only do this if you would like to spend a few dollars a year extra to support your Amateur Society. You may like to support us if you're pleased that you can become a licensed Amateur at 15 now, you now only have to pass 10 w.p.m. c.w., you now can use 400 watts p.e.p. s.s.b. output, you can now go portable or mobile for five days without prior permission, you can now officially use unmanned v.h.f. repeaters under certain conditions, and because you can, in short, enjoy quite liberal operating conditions.

The gaining of those privileges and others over the past few years has been because your society is held in high regard by the administration, and because it represents (just) over 50% of Amateurs. Very soon we may have to "represent the Amateur Service" very strongly in reference to v.h.f. frequency spectrum allocations. It would be a great source of strength if we represented 60% or 70% or all Amateurs, active or inactive.

Are you a long-time member? Then please show this to a friend who is a call sign holder, but inactive. He may like to receive the magazine. Please note, however, that for all of you, the direct subscription to the magazine will cost less than W.I.A. membership, but is the saving really worth it?



John Batrick, VK3OR

AN EXPERIMENTAL 455 Kc. I.F. STRIP

E. MANIFOLD.* VK3EM

ONE would think that by now everything that could be written about i.f. amplifiers would have been covered in some way or another, but it seems that there are still ways of using available units to produce better results, any information available not having been circulated to any extent. There is nothing new in the fact that ceramic filters can be used in i.f. stages, having been done many times, but to date very few designs have used them in cascaded stages utilising the double ring-dot type of resonators.

Where these filters have been used in cascaded stages practically no information has been given as to the pass-band selectivity, except one article¹ (also Refs 2 and 3) did mention that "good skirt selectivity with reasonably square flat-topped response" was available.

To original thoughts and queries on this subject, no answers were readily available, but in line with tuned circuit characteristics where by increasing the number of cascaded stages, a narrower bandpass and steeper skirt selectivity is produced, particularly at frequencies of 50-100 Kc., it was thought that similar results could be produced by cascaded ceramic filter stages.

Looking at the selectivity curves for "Murata" SF455D ceramic filter units in single stages (Fig. 4), shows that the peak of the curve is reasonably sharp and is adjustable over fairly wide limits with different coupling condensers, but the skirt selectivity leaves much to be desired, definitely not satisfactory for a communications type receiver by modern standards.

All the foregoing thoughts had been provoked by the fact that Ric Hill VK3RC, had made available several SF455D and BF455A "Murata" ceramic filter units from I.R.H. Components Pty. Ltd. for experimental purposes. Unfortunately, the project has been delayed due to the pressure of other duties and has only now become a reality.

A p.c. board was laid out and prepared with parts assembled to the circuit of Fig. 1, using NPN germanium transistors, only because these were at hand, although other circuits for these filter units show silicon transistors as being used, as in Fig. 3, which should be low to medium gain types to avoid instability.

For this reason no resistor values have been shown on Fig. 1 for base and emitter bias resistors as they will vary, depending on the type of transistor used, and as it does not affect the final result to any extent they were not included.

As this was an experimental set-up, no a.g.c. circuitry was included, the main consideration being the selectivity, stability and gain of the strip, using the "Murata" ceramic filter units and by-passes for three stages of i.f.

It was realised at the outset that each filter unit may, or may not, be exactly the same frequency at 455 Kc., but it was hoped that the spread over the three units would not be excessive, and proved to be an average centre frequency of 454.8 Kc. for the experimental strip, for these three units.

VARYING THE COUPLING

When first assembled the coupling condensers between pins 1 and 2 on each filter unit were all 25 pF, on the assumption that it would produce a curve at 2 Kc. bandwidth, similar to the published curves for a single stage (Fig. 4), but with steeper skirt selectivity.


Certainly the skirts were much steeper but the nose of the curve was also much sharper (curve No. 4, Fig. 2) and was only suitable for c.w. operation, being approx. 0.6 Kc. at the 6 db. point and 2 Kc. at the 40 db. level, the limit of measurement at this location.

Single signal selectivity indeed, as by a listening test, placing the b.f.o. on either side of the i.f. passband only half of the signal was copiable, the other sideband being just audible when tuning over the signal.

Unfortunately this is where the difference in each filter unit becomes noticeable, as the curve plotted for this arrangement was slightly asymmetrical due to the different frequency of one unit.

The next test was to go to the other extreme and fit 150 pF. condensers in place of the 25 pF. condensers across pins 1 and 2 of the filter units, the result being indicated by curve No. 1 Fig. 2 with a 4.5 Kc. bandpass at 6 db. and 8.5 Kc. at the lower extreme.

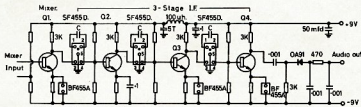This was considered as being too broad for the present s.s.b. requirements, so the 150 pF. condensers were replaced with 100 pF. condensers to produce curve No. 2 (Fig. 2) which, while very good for a.m. operation, was



C-See FIG.2. *T*-Tantalum condenser,
FIG.1. CIRCUIT OF CERAMIC FILTER I.F. STRIP

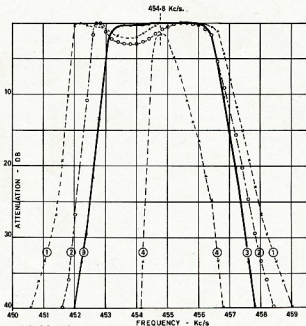


FIG. 2.-3 Stage 1F. Response curves

* 267 Jasper Road, McKinnon, Vic., 3204.

THE QUESTIONNAIRE - SOME FURTHER PROGRESS

Before proceeding with further analysis, we would mention that a few late replies have arrived, sufficient to raise the over-all return to 31.2% a little under a 1% increase. A few trial runs showed that the extra replies made practically no difference to the figures already compiled, hence it was decided not to re-work the vast number of calculations already made. These late returns have been retained in order that the comments included in them may be taken into consideration at a later stage of our investigations.

The subject of readers' requirements took a considerable amount of "crystal gazing" as comments left some answers in doubt. These we have classified as "maybe". Some made no attempt to answer the question, so have been omitted from the figures.

The summary gives us the following table:

	Yes	No	Maybe
	%	%	%
Technical articles	98.3	1.3	0.4
DX Notes	47.5	51.5	1.0
VHF Notes	52.5	46.2	1.3
Federal Notes	60.0	23.4	16.6
Divisional Notes	50.5	45.5	4.0
SWL Notes	23.4	75.5	1.1
Trade Reviews	71.5	27.9	0.6
Book Reviews	59.0	40.5	0.5
Correspondence	61.5	36.8	1.7

In VK1-2, VK5-8 and VK7, the majority did not want the DX Notes, while in VK3 exactly the same number voted for as did against. The other two Divisions had a majority in favour of DX Notes by only very narrow margins.

In VK4-9 and VK7 the majority voted against the VHF Notes, again the margins were very small, being less than 2% difference.

All States voted in favour of Federal Notes, and some most enlightening comments were included. In due course, these comments will be extracted and forwarded to the Federal Executive for their consideration and action where thought necessary.

The Divisional Notes appear to be the strongest bone of contention. As the table shows, the voting was fairly even, so much so that in VK3 and VK4-9 the "no" majority made it by only one vote. VK7 was also against, but by a wide margin. The most frequent comment by those in favour, stipulates the Divisional notes should not be in the old form, but should be restricted to items of general interest, such as reports of meetings and future activities, with personal "pars" eliminated. Those against, in the main, consider that all Divisional matters are best left to Divisional bulletins and broadcasts.

No State favoured SWL Notes and the only surprise in this section was the noticeable lack of support by the SWLs and Associates themselves. Many with call signs, although indicating SWL Notes should be included, indicated they had no personal interest themselves, but felt they would be of use to others. On this matter, we will have more to say later, when we review the many comments in more detail.

All States except VK7 are in favour of Trade Reviews, only 33% of their votes being in favour. Many interesting comments were made regarding the types of review, and these will be taken into consideration later.

VK6 voted against Book Reviews by a margin of 3%, while all other States were in favour by fairly high margins. VK7 was again the odd-man out on the subject of correspondence with a 3% majority being against the correspondence section.

Readers' preferences appear most interesting and more work has to be done on this matter. As far as we have gone, we find the first choice to be:

VK1-2	Antennas
VK3	Receivers
VK4-9	Receivers
VK5-8	Receivers
VK6	Transmitters
VK7	Receivers

On an Australia-wide basis, the first choice figures are:

Antennas	25.4%
Audio Equipment	0.9%
Hints and Kinks	11.9%
Receivers	26.6%
Test Equipment	12.5%
Transmitters	22.5%

As to how we finally evaluate this information and how best to use it, has yet to be decided, but for certain, we will not be wasting space on audio equipment, unless it is strictly orientated towards Amateur Radio applications.

As far as the question on advertisement perusal is concerned, there is no point in making any calculations. Well under 1% would have indicated they did not read them, and possibly under 5% only look at some of them. This matter has been commented on at great length in the "any other suggestions" portion of the questionnaire. Some suggestions are completely impracticable, but this was only to be expected. However, we did find some wheat amongst the chaff, and we have already acted on some of the sound suggestions received. Some of the suggestions we would like to act on, and in these cases we can only pass them to the advertisers for their consideration. To all those who adversely commented on certain advertising material, we can only draw attention to the fact that we had already taken action on this matter at the time the questionnaire was published, and such type advertising has not appeared in recent months.

A point frequently raised is the lack of advertising from the "smaller" States. This is a matter that has been raised at Federal Conventions for many years when attention has been drawn to the Federal Policy Book, item M06, which states:

"That there shall be appointed in each Division a sub-editor of 'Amateur Radio' who will be responsible within the Division for—

- (a) Collation of Divisional Notes.
- (b) Procurement of technical articles.
- (c) Furthering the circulation of the magazine within his Division.
- (c) Collaborating with the Publications Committee in increasing the volume of advertising in the magazine."

This policy item was framed back in 1947 and after 22 years has never been taken seriously by any Division, therefore any complaints regarding lack of advertising from certain States should rightly be directed to the Council of the State concerned for their action.

The whole matter of advertising is a complex one and it may help if some few details are clarified. There is the impression that advertising is a highly profitable operation for the magazine. While there is some profit in it, it is not large. In setting advertising rates, factors such as circulation and likely return for the expense must be considered, as well as production costs. In an earlier report, we gave estimates of the national level of spending on our hobby, and it must be admitted the average figure for each Amateur is not high. To encourage more advertisers, we must either spend more individually or increase the number of active Amateurs to increase the size of the market. As the position stands now, we are of the opinion that the new rates we have had operating since January are fair to all concerned.

Literally hundreds of suggestions were received which would improve the magazine, but only by greatly increasing the costs of production. For this reason they cannot be seriously considered at this time, but could be incorporated as part of a long-range programme. For example, a popular suggestion was that the size of the magazine should be the same as "QST" and similar publications. This suggestion has been considered for at least the last ten years, but as it is more expensive than the present size, we cannot make the change. Going through our library, it is noticeable that the American publishers are the main exponents of the smaller format, while the Societies with smaller circulations prefer the larger format. It would appear they also use larger formats for economic reasons.

We wholeheartedly agree with all those who asked for photos and descriptions of stations of other Amateurs. Some years ago we did have such a section, but for some reason the supply of suitable material dried up. Odd ones have been directed to us over the years, but very few have been suitable for reproduction. If Divisional sub-editors (???) would like to follow this one through we will go along with it. Two from each Division will keep us going for a year. If we are rushed with offers, publication will be made in State numerical sequence from 2 to 7, one at a

(Continued on Page 18)

drain in the event of short circuits or component failure.

The 1,000 uF. capacitor across the unregulated input improves both the filtering and the dynamic regulation of the supply.

The rest of the regulator module is devoted to the various change-over, gating and adjustment functions required by the transceiver. They will now be described.

(i) The unregulated supply voltage is applied only to the receiver audio module and to the transmitter p.a. Both of these functions have wide current demands and are best separated from the remainder of the modules in the interests of economy and stability.

RLIA applies unregulated voltage to the receiver audio module when in the unenergised "receive" condition and to the p.a. board when energised through the p.t.t. or other tx/rx switch.

(ii) The injection mixer and filter modules are energised at all times and thus are supplied straight from the regulated output. According to the frequency required, one of the heterodyne crystal oscillators must be in operation at all times and is thus supplied straight from the regulated line via the band switch.

(iii) The regulated d.c. line is connected to the change-over contacts of RL1B. In the unenergised receive position, voltage is applied to the receive only functions via the gating diodes D18 and D19. At the same time no voltage is applied to the base of the "S" meter switching transistor so that it is open circuit and allows the "S" meter circuit to function. When energised on transmit, the relay contacts apply voltage to the "transmit only" functions through the gating diodes D16 and D17. Voltage is also applied on transmit to the base of the meter transistor switch, pulling it hard on and isolating the "S" meter circuit.

(iv) In the transmit position regulated voltage is applied via D16 straight to the balanced modulator and to the various transmit mixer/pre-amplifiers via the band switch. The line through D17 goes to the two-pole four-way switch which is used to select either the internal v.f.o. or alternative external frequency control facilities. D17 also gates a supply to the b.f.o. at all times.

(v) In the receive condition, D18 gates supply voltage through the internal/external switch to the v.f.o. and to the b.f.o. via the a.m./s.s.b./c.w. function switch. Note that the b.f.o. is always energised on transmit, but on receive only it may be made inactive when receiving a.m.

D19 gates supply to the receiver i.f. strip and to the (optional) crystal calibrator on receive. Note that the receiver front-end supplies are obtained from the a.g.c. line via the bandswitch, and that the product detector supply comes from the gating diodes in the b.f.o. (refer to Fig. 12 in Feb. 1969 "A.R.").

The four gating diodes D16-19 are used to prevent transmit functions being energised on receive (and vice-versa) through the interconnections of the internal/external frequency control switch.

(vi) "S"/Power Out Meter

The meter used is a simple 0-1 mA. instrument and is used to indicate both the relative strength of the received signal or the relative power output of the transmitter. Change-over switching is automatic.

The meter type in the project is the one advertised by Ham Radio Supplies, of 323 Elizabeth St., Melbourne, 3000. It is ready calibrated in (arbitrary) S units.

On receive, the relative signal strength is indicated by comparing the a.g.c. rail voltage with that of the regulated supply rail. As the signal strength increases, the a.g.c. rail voltage falls and the voltage across the meter rises. The meter is thus forward reading. The no-signal voltage across the meter is set to zero by means of

that this description be read in conjunction with the back articles.

Note that all signal wiring between the boards is done with small diameter co-axial cable for r.f. and with shielded cable for audio.

The signal from the antenna goes via the antenna change-over relay (RL2) through one section of the bandswitch to the link coils on each receiver front-end board. The 9 Mc. outputs from each board are all paralleled and taken to the filter pre-amplifier. Note that the filter pre-amplifier also accepts signal from transmitter balanced modulator and that the signal change-over is done on the filter pre-amp. board by means of a diode (D6).

On both receive and transmit, the output of the filter pre-amp. is taken to the filter board from which it goes

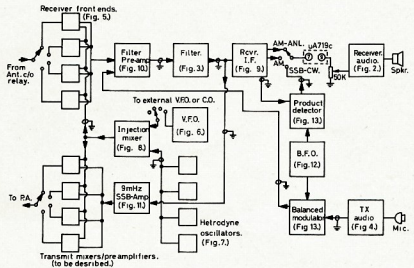


FIG. 15. 4 BAND TRANSISTOR TRANSCEIVER - Signal interconnections.

the 2K tab pot, while the 22K in series with D20 is used to set the full scale deflection of the meter.

On transmit, voltage is applied to the base of the 2N3564, switching it hard on and effectively grounding the a.g.c. line. Rectified r.f. from the p.a., negative going in polarity, is compared with the voltage on the regulated supply rail to give a forward reading indication of power output. The 22K tab pot in series with D21 is used to set the full scale reading of the meter. The two diodes D20 and D21 are needed to prevent interaction between the two negative supplies to the meter.

SIGNAL INTERCONNECTIONS

Fig. 15 shows the signal interconnections between the various modules of the receiver and some of those for the transmitter. The references on the various modules are the figure numbers given in "A.R." since the series started in November 1968. It is recommended

either to the receiver i.f. strip or the 9 Mc. transmit amplifier. Selection of the signal path is effected by means of diode D9 on the 9 Mc. amplifier board.

There are three outputs from the i.f. strip—am. (not limited), a.m. (limited) and a 9 Mc. s.s.b./c.w. outlet to the product detector. The first two (audio) outlets go to two of the three switch positions, with the third position accepting audio from the product detector.

The product detector, b.f.o. and balanced modulator are housed together in a die cast box, the output of the b.f.o. being connected inside the box to the product detector/balanced modulator board. Fig. 14 shows how h.t. is applied either to the p.d. or b.m. to select the required function.

Audio from the mode selection switch is amplified in the spare section of the uA719C 9 Mc. amplifier on the

i.f. board before passing to the receiver audio module via the audio level control. This will be explained more fully below.

Returning to the front-end of the receiver, the outputs from the four (or more) heterodyne crystal oscillators are applied in parallel to the injection mixer. The appropriate crystal oscillator is selected by switching h.t. to it (see Fig. 14). The v.i.o. output or one of the external frequency control sources is applied to the injection mixer, the output of the mixer being applied at all times to the paralleled inputs of the four rx front-end boards and the four transmitter mixer/pre-amp. boards. Once again selection of the required function is made by applying h.t. to the appropriate p.c.b. via the bandswitch.

Output from the 9 Mc. s.s.b. amplifier is applied to the four paralleled inputs of the transmit mixer/pre-amp. boards.

Band switching in the receiver has thus been reduced to a single bank with most of the frequency selection being done via the h.t. line.

The treatment of the audio outputs from the i.f. strip and product detector may need expansion.

A spare "transistor" is available on the uA719C in the i.f. strip and this is used to provide additional a.f. amplification before the main audio module.

The required audio output (a.m. unlimited, a.m. limited, or s.s.b./c.w.) is taken from the wiper arm of the function switch straight to pin 7 on the uA719C. Output is taken from pin 9 of the i.c. In the project p.c.b.s these spare pins are made readily available on the top of the p.c.b. by use of terminal pins.

Output from pin 9 is taken direct to the top of the 50K audio level control, the slider of which goes direct to the input points on the audio module.

After the rest of the tx modules have been described, the balance of the signal interconnections as they apply to the remainder of the transceiver will be detailed.

AVAILABILITY

The voltage regulator boards and kits will be made available in the usual way by application to one of the authors the price being \$16.60 plus 20c postage for the full kit. Boards will be separately available at \$2.00 each plus 5c postage.

ERRATUM

It is regretted that an error appeared in the January issue. Fig. 9 shows that the input to the uA719C is with the coil tap going to pin 2 and the de-coupled side of the input going to pin 1.


These connections should be reversed with the "hot" input from the coil going to pin 1 and the "cold" or de-coupled side to pin 2.

CHOOSE THE BEST—IT COSTS NO MORE



O. T. LEMPRIERE & CO. LTD. Head Office: 31-41 Bowden St., Alexandria, N.S.W., 2015
and at Melbourne — Brisbane — Adelaide — Perth — Newcastle

AIR-WOUND INDUCTANCES

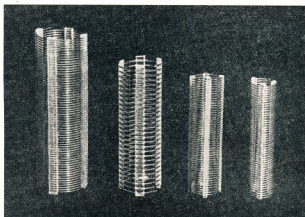

No.	Diam.	Turns per Inch	Length	B. & W. Equiv.	Price
1-08	1/2"	8	3"	No. 3002	66c
1-16	1/2"	16	3"	No. 3003	66c
2-08	5/8"	8	3"	No. 3006	76c
2-16	5/8"	16	3"	No. 3007	76c
3-08	3/4"	8	3"	No. 3010	91c
3-16	3/4"	16	3"	No. 3011	91c
4-08	1"	8	3"	No. 3014	\$1.04
4-16	1"	16	3"	No. 3015	\$1.04
5-08	1 1/4"	8	4"	No. 3018	\$1.28
5-16	1 1/4"	16	4"	No. 3019	\$1.28
8-10	2"	10	4"	No. 3907	\$1.68

SPECIAL ANTENNA ALL-BAND TUNER INDUCTANCE

(equivalent to B. & W. No. 3907-7")

7" length, 2" diameter, 10 turns per inch, \$3.00

References: A.R.R.L. Handbook, 1961; "OST," March 1959; "Amateur Radio," December 1959.

Take the hard work out of Coil Winding—
use "WILLIS" AIR-WOUND INDUCTANCES

WILLIAM WILLIS & CO. PTY. LTD.

430 ELIZABETH ST., MELBOURNE, VIC., 3000.

Phone 34-6539

The W5OMX Communications Receiver*

Single-Conversion Superhet with Good Stability

COL. DAVE CURTIS,† W5OMX

LONG-TIME "QST" readers will recall WIDX's excellent article on receiver design in the January, 1957 issue.¹ At the time it appeared, the article was studied with great interest. Particularly, the point that selectivity belongs as close to the antenna as possible seemed to make a great deal of sense. With the appearance of high frequency filters at reasonable prices, the author initiated the design of a receiver to utilize this principle. For various reasons, however, this receiver never got beyond the block-diagram

● As communications receivers go, this one is reasonably simple and straightforward. It combines some of the best features of previous designs, including a high frequency crystal filter for s.s.b. selectivity, an audio filter for c.w. selectivity, a beam-deflection mixer, dual detectors, audio-derived a.f.c., and a temperature compensated v.f.o.

PERFORMANCE

In more useful specifics, here is how the receiver stacks up:

Sensitivity: Very f.b. Digs right down to the noise level on all bands, 80 through 10 metres. The receiver has made possible R5 copy of both ends of a W6/W2 QSO on 40, and of a KL/W4 QSO on 20, using only a finger touching the input connector as an antenna!


Stability: Truly marvellous. From a cold (room temperature) start, drift is inconsequential after a 15-minute warm-up. Further, the switching arrangement permits leaving the filaments on continuously. When this is done, and heat soaking has occurred, there is no apparent drift after the mode switch is turned to the appropriate "on" position. If there is any drift, it is the other guy!

Selectivity: About right for s.s.b. Gives good single signal selectivity on c.w.

Mechanical: Can take sharp raps with no noticeable frequency shift.

Birdies: A few. There are one or two of consequence on each band segment, except on 15 metres where there are six (by actual count). These tune sharply, and seldom bother reception. Nevertheless, this is a basic design deficiency which, perhaps, could be overcome by someone who is mathematically inclined and who can select conversion frequencies more intelligently.

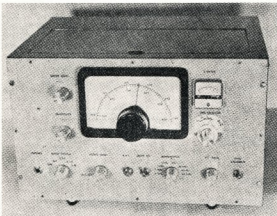A.g.c.: The circuit suggested by WIDX² is the best we have seen. S.s.b. signals ranging from S2 or 3 to 10 over 9 come out of the speaker at quite reasonably similar levels. This is one a.g.c. that will be used most of the time.




The W5OMX Receiver. Main tuning dial (J. W. Miller, MD-7) has both 6:1 and 36:1 tuning ratios. A 6:1 planetary drive assembly (Arrow Electronics, Type 4511) is used on the pre-selector tuning capacitor. The pointer is home-made.

stage. A more recent article by WIDX,³ which was illustrated with an operational piece of hardware, provided the final push. Serious design and construction followed, and the "W5OMX" receiver, described here, is the result. It is a spectacular performer.

Unfortunately, the author's shack is not equipped with test gear adequate to permit performance measurement. Consequently, resort had to be made to subjective comparison, and the opinions of fellow Amateurs. These judgments suggest that the double-conversion receiver, utilizing a low frequency second i.f. to obtain selectivity, may be on the way out. The author's second receiver—a 16-tube double-conversion job of sound design—simply cannot compete. In side-by-side tests, using a common antenna the contrast is remarkable. The new receiver performance is characterized by a clarity in signal quality, the result of a markedly lower overall noise level. Signals masked to unintelligibility

by noise in the older receiver become readable copy. In conditions of reasonably low atmospheric noise, signals appear to pop out of surrounding quiet.

V.f.o. assembly with the slide-top cover removed. The 8AU6 socket and associated components are at upper right with the band-set capacitor C7 at lower right. The coil is glued securely to a ceramic stand-off insulator. The differential capacitor, C8, with temperature compensating capacitors C9 and C10 attached, is at upper left. Note that all major components and tie points are fastened securely to the same side of the enclosure for maximum mechanical integrity. When mounted on the chassis the right-hand end of the box in this view is at the top, the left-hand end is bolted to the chassis.

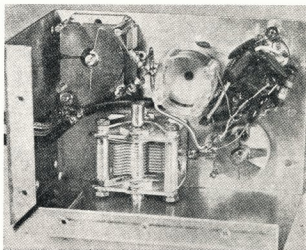

* Reprinted from "QST," January, 1968.

† 29 Outer Octagon, Randolph AFB, Texas 78148, U.S.A.

¹ Goodman, "What's Wrong with Our Present Receivers?" "QST," January, 1967.

² Goodman, "Some Thoughts on Home Receiver Design," "QST," May, 1965.

CIRCUIT OUTLINE

Interested? Let's have a look at the schematic of Fig. 1. As far as the signal is concerned, this is a single-conversion receiver. The incoming signal is amplified in the single r.f. stage using the pentode section of a 6AZ8. It is then converted to an i.f. of 9 Mc. in a 7360 mixer. A band 2.8 Kc. wide is sliced out by a steep-stepped crystal filter, FL1. The signal is then amplified through three i.f. stages using 6BA6s, and finally detected by an infinite impedance detector, V3B, i.f. a.m., or by a 6BY6 product detector, i.f. s.s.b. or c.w. The otherwise conventional audio system includes a selective filter for c.w. work. The a.g.c. system is audio derived.

The main tuning element is the v.f.o., covering 5 to 5.5 Mc. Bands are changed by altering the frequency of local injection to the signal mixer. This is accomplished by heterodyning signals from the v.f.o. and from the crystal oscillator V2A to produce the required injection frequency in the output of the heterodyne mixer, V2B. A 3.5 Mc. crystal oscillator, using the triode section of the 6AZ8, provides markers for the low frequency edges of the bands covered.

THE V.F.O.

The v.f.o. is a 6AU6 in a very high-C Colpitts configuration. A differential capacitor, C8, in combination with NP0

and N750 fixed capacitors, permits simple and accurate adjustment of temperature compensation. With reasonable attention to mechanical design, and careful adjustment, stability is impressive indeed. This circuit was used in an earlier project,³ and was found to provide stability comparable to that of the BC-221 frequency meter. No small part of the stability is due to the use of the rugged low-torque Miller tuning capacitor.

R.F. STAGE AND CRYSTAL CALIBRATOR

Air wound coils are used in the pre-selector. The gain in this stage appears to be approximately 12 to 15 db. on 80 and 40, dropping off to about 6 to 8 db. on 15 and 10. It does a good job of rejecting i.f. images (none have been found). With some antennae, the gain of this stage may have to be reduced slightly to prevent oscillation on the 80 metre band; on other bands the amplifier is perfectly stable at full gain. Input and output circuits are gang-tuned. Ceramic trimmer C1 (one for each input coil) is used to adjust the tracking.

The triode section of the 6AZ8A, V1B, is used in the crystal calibrator. The frequency can be "zeroed in" against a calibrating source by means of C4. Notice that the 15 metre band

and all ranges of the 10 metre band are covered with a single set of pre-selector coils.

SIGNAL MIXER

The 7360 performs the mixing function effectively, and contributes inconsequential noise. It does not appear to overload on even the very strongest signals. The mixer gain control, R2, is used to prevent oscillation on 80 metres, and to adjust the overall gain on the other bands. By adjusting the gain at this point, the high gain i.f. strip may be operated at full amplification at all times for optimum a.g.c. action.

I.F. AMPLIFIER

Since selectivity is provided ahead of the i.f. strip, these stages are designed purely for amplification. The 24 pF. capacitors across the hot ends of the i.f. transformers increase the overall gain spectacularly. A 0.2 volt signal at 9 Mc. injected into this strip ahead of the crystal filter comes out at a whopping 20 to 25 volts. This accounts in a large measure for the rather impressive overall sensitivity of the receiver. The i.f. gain control, R3, is used only during initial adjustment and testing; therefore it is not mounted on the panel, but on the rear apron of the chassis.

DETECTORS

The 6BY6 product detector, developed by W6TC for his very efficient HBR

- C1-212 pF. ceramic trimmer (one for each L2 coil).
- C2-Load section air variable, approx. 50 pF. per section.
- C3-See coil table.
- C4, C12, C13-Approx. 12 pF. compression trimmer.
- C5-See coil table.
- C6-100 pF. variable.
- C7-30 pF. air trimmer.
- C8-See differential capacitor.
- C9-22 pF. NP0.
- C10-22 pF., N750.
- C11-See coil table.
- CR1-CR4, Incl.-Silicon diode, 400 p.i.v., 100 mA.
- CR5, CR6-Silicon diode, 200 p.i.v., 175 mA.
- FL1-9 Mc. crystal filter (McCoy Silver Sentinel).
- J1-Chassis mounting co-axial receptacle.
- J2-Open circuit jack.
- J3-Closed circuit jack.
- L1-L7, Incl.-See coil table.
- L8, L9-Filter choke.
- L10-0.5 h. toroid.
- M1-S meter.
- R1, R2, R3, R5, R6, R7-Line control.
- R4-Audio taper control, S3 attached.
- RFC1-24 turns No. 26 wound on 470,000 ohm VSW resistor.
- RFC2-Same as RFC1.
- RFC3, RFC4, RFC5, RFC6-2.5 mH r.f. choke.
- RFC7, RFC8-1 mH r.f. choke.
- S1-7-section 7-pole 8-position ceramic rotary switch.
- S2-S.p.s.t. toggle switch.
- S3-S.p.s.t. switch (see R4 above).
- S4-3-section 6-pole 8-position ceramic rotary switch.
- S5-D.p.d.t. toggle switch.
- T1-9 Mc. input transformer.
- T2-9 Mc. output transformer.
- T3, T4, T5-10.7 Mc. interstage transformer. Mount with spade bolts.
- T6-Power transformer, 550 volts r.m.s., centre tapped, 110 mA.; 6.3v. 5 amp.
- T7-2 watt audio output transformer (5000 ohms to voice coil).
- T8-Transistor audio input transformer, 5000 ohms to 7500 ohms, centre tapped.
- V1-See coil table.
- V2A-6AU6 v.f.o.
- V2B-6AU6 heterodyne mixer.
- V3B-6BA6 i.f. amplifier.
- V4-6BA6 i.f. amplifier.
- V5-6BA6 i.f. amplifier.
- V6-6BY6 product detector.
- V7-6AZ8A r.f. amplifier and crystal calibrator.

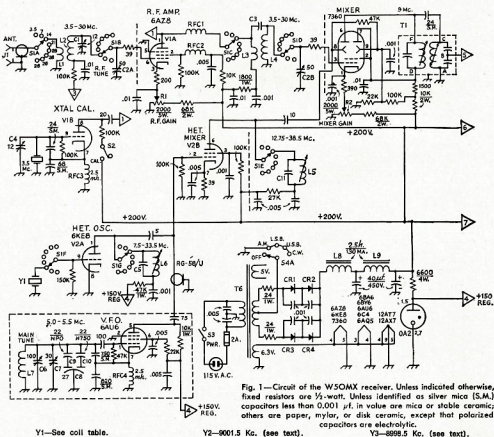


Fig. 1—Circuit of the W50MX receiver. Unless indicated otherwise, fixed resistors are 1/2-watt. Unless identified as silver mica (S.M.), capacitors less than 0.001 μ f. in value are mica or stable ceramic; others are paper, mylar, or disk ceramic, except that polarized capacitors are electrolytic.

receivers,* works well at 9 Mc. This circuit has the very desirable feature of accepting a wide range of signal levels with little or no apparent distortion in the audio product. The infinite impedance detector provides these same advantages in a.m. reception, without overloading the last i.f. transformer as would a diode.

B.F.O.

The b.f.o. uses the two triode sections of a 12AT7 as separate crystal oscillators. The crystals at 8001.5 and 8998.5 kc. (supplied by McCoy with the filter), permit selection of lower and upper sidebands, respectively, by keying the appropriate 12AT7 cathode. These crystals are adjusted to proper frequency by trimmers C12 and C13.

AUDIO SECTION

Three stages of audio provide generous output to high impedance phones or a speaker. You can hear signals on this receiver over the QRN of all but the noisiest "harmonics"! In the c.w. mode, a high-Q audio filter, composed of toroid L10 and its related capacitor, permits peaking the beat note at approximately 1,000 cycles. Substitution of a different value of capacitance will move the resonant frequency to your choice of pitch. Selectivity may be varied by adjustment of R7.

4 "Hints and Kinks," "QST," June, 1962.

A.G.C.

The a.g.c. circuit amplifies and full-wave rectifies audio from either detector, and controls the r.f. amplifier and all three i.f. stages. It is remarkably effective, and makes the multi-party s.s.b. ragchew a real pleasure. (Those who enjoy fiddling with knobs probably won't like it!) The fast-attack/slow-decay characteristics which result from the component values suggested by WIDX have proven to be very close to the ideal.

The S meter and power supply circuits should be familiar to most readers. S meter adjustments are made at the rear of the chassis. Silicon rectifiers are used in the power supply, and a voltage regulated tap supplies the v.f.o. and heterodyne oscillator.


MUTING

You will note that no provision for muting is indicated in the circuit schematic. Three possible arrangements are suggested. Your choice should be based upon how you intend to connect the receiver into the overall station set-up. If you intend to monitor your transmissions on the receiver, and use an antenna relay that grounds the receiver input on transmit, break the plus B or cathode connection of V1A, and insert the muting switch and remote connections at this point. If you have side-tone monitoring, you can cut off the receiver entirely by breaking the plus B or cathode connection of the 7360 mixer, and inserting the mut-


ing connections at that point. Finally, and perhaps the best of all, although additional components will be required, use the muting arrangement suggested by WIDX.²

CONSTRUCTION

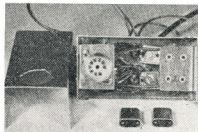Viewed in its entirety, the construction of a receiver of this complexity may appear to be an overwhelming task. Certainly, it would be a very ambitious first project. However, for anyone with sufficient experience and skill to do the minor fabrication and locate



B.f.o. assembly with tube, cover and crystals removed. The sockets for the crystals and the 12AT7 are mounted on small aluminum brackets, the small components underneath being wired prior to final assembly. The crystals are plugged in internally and require no clearance holes in the cover. Crystal trimmers C12 and C13 are fastened to the bottom of the Minibox enclosure, at the centre. The shielded leads and output co-ax. cable leave the enclosure through tightly fitting holes to minimise r.f. leakage.

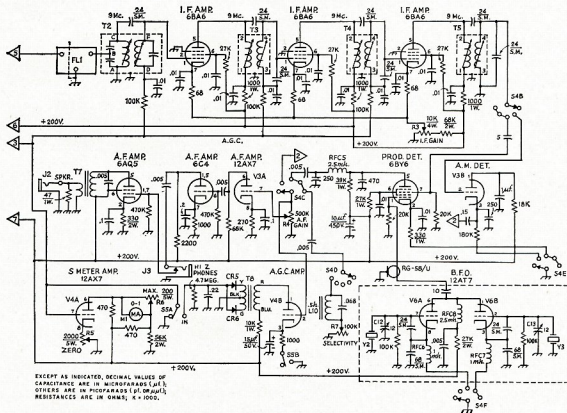

sensibly the many small components, it should be a feasible undertaking. The primary ingredients of successful homebrew construction seem to be patience, a willingness to take one step at a time, and the interest to keep going. If you have these talents, you can probably build a receiver of the same superlative performance as the one described. And it should be better looking; this one is the final result of many, many component substitutions in the search for optimum performance.*

The following paragraphs contain construction and alignment suggestions, roughly in the order followed by the author. Additional information may be obtained by a careful study of the several illustrations and accompanying explanatory captions.

The receiver is built on a 10" x 14" x 3" aluminium chassis which fits into the 11" x 15" x 9" cabinet. An additional 10" x 17" x 3" chassis (the smallest size obtainable made from 16 gauge stock) was purchased as a source of shielding partitions. The material for the v.f.o. enclosure and shielding partitions.

ASSEMBLING THE V.F.O. AND B.F.O.

Make the v.f.o. first. The main part of the enclosure was made from a corner of the spare chassis. Its dimensions are 4 1/2" x 3 1/2" x 3". The side/top cover was cut from adjacent spare chassis material. (The rear of the box is left open.) Mount the major components all on one side of the box, as shown in the detail photograph, to minimise frequency changes with mechanical stress. Care should be used in locating the tuning capacitor so that its extended shaft will be high enough above the chassis to clear the McCoy filter in the i.f. strip (see top chassis photograph), and yet not be so high that it will crowd the dial too close to the upper edge of the panel.

The b.f.o. components are assembled in a 1 1/2" x 2 1/2" x 4" Minibox. Construction is detailed in one of the photographs.

BAND SWITCH

Before starting to lay out the component pattern on the chassis, the under chassis shields should be cut, using material from the aprons of the spare chassis. The longer shield has a length of 8 1/2"; the other two are 7" long. Then they should be placed temporarily in the chassis while their positions are adjusted. Space them apart suitably to provide adequate room for the coils, and measure the spacing accurately.

Make a mark on the rearmost shield, indicating the distance that the switch shaft will be placed from the end of the chassis. Mark and drill the switch-shaft and mounting holes in the three partitions, using extreme care to see that they are as identically located as possible. Make the holes reasonably oversized. Then assemble the switch and shields as a unit, using spacers on the switch assembly rods to obtain the partition spacings measured earlier. Do not tighten the assembly nuts more than

finger tight. Place the assembly in the chassis, and press down firmly on the shields while the assembly nuts are tightened. Spot the shield mounting holes, remove the assembly, and drill the holes.

Avoid any mounting holes in the area that will be occupied by the v.f.o. box, since this box must rest flat on the chassis. (The b.f.o. assembly can be raised on spacers to clear any mounting screws in its area.) Additional holes that should be drilled in the shields are one in each of the shields, below and to the left (in the bottom view) of the switch wafers (for wires), one in the upper left-hand corner of the second shield, and another in the same relative position in the first shield (for tie-point strips). A 3/8" hole should be drilled in the first shield, to the left of the short vertical shield. This will be used to pass the co-ax. feed line from the v.f.o. to the heterodyne mixer, and some of the power leads. The corners of the partitions that rest in the fold of the chassis should be cut off to allow passage of wiring between the panel and the rear of the chassis.

CHASSIS LAYOUT

Once the shield locations have been determined, the positions of the two main rows of components will become apparent. With the v.f.o. subassembly placed with its rear edge flush with the rear edge of the chassis, and the shaft of the tuning capacitor central on the chassis, the location of surrounding components can be spotted. In locating the preselector tuning capacitor, place it far enough toward the edge of the chassis to assure space for its dial on the panel.

After all hole centres have been marked and hit with a centre punch, the various holes may be drilled or cut. The author used a nibbler to cut the i.f. transformer holes to approximate size, and finished up with a file.


Before mounting any components on the chassis, fasten the panel temporarily in place, and place the shafts of the v.f.o. and preselector tuning capacitors against the back of the panel while you mark the shaft heights.

WIRING

Tie-point strips should be located liberally on the underside of the chassis, convenient to tube sockets and related components. It is advisable also to place grounding solder lugs on most of the mounting screws. You may not use all of them, but it is much more convenient to install them as you mount the components than later on when space becomes scarce as the wiring progresses.

Power supply and filament connections should be made first. Thereafter, the wiring procedure is not particularly critical. Installation of the preselector coils can be left as a last operation, after the v.f.o. and b.f.o. circuits have been adjusted. To make sure that no connection is overlooked, it is a good idea to mark the schematic with a coloured pencil as each connection is completed.

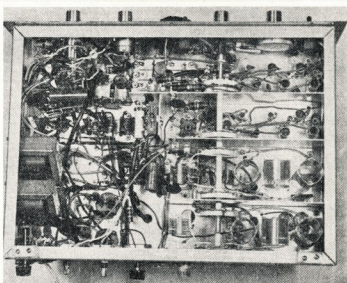The author wired the front circuits first, working toward the rear of the chassis. Following standard practice, long leads, particularly those connecting front-panel controls and switches to components at the rear of the chassis, may be made with shielded wire. This practice permits fastening the leads



Bottom view showing band switch and coil compartments. The pair of close-spaced wafers at the top switch the heterodyne-oscillator coils and crystals. The single wafer below switches the heterodyne-mixer coils. The signal-mixer coils are in the next compartment, switched by the pair of widely-spaced wafers. R.F. stage coils are in the bottom compartment; one of the two switching wafers is hidden by the lip of the chassis. The 40 and 80 metre air-wound coils are cemented to platforms made of polystyrene sheet. The higher frequency coils are supported on switch terminals. The mode switch is in the upper left-hand corner, filter chokes in the lower left-hand corner. A.g.c. components are mounted on tie points on the short vertical shield near the centre.

*To assist those who wish to duplicate this project, the author will provide full-size templates for chassis and front panel, an enlarged schematic complete with part list, and 8 x 10 inch enlargements of the four primary illustrations, at a cost of \$4.50 post paid.

COIL TABLE

L2, L4									
Band	Turns	Wire Size	Diam. Inch	T.P.I.	L1 Turns	L1/L2 Space	L3 Turns	L3/L4 Space	C3 pF.
80	50	24	1	32	6	2 t.	6	10 t.	None
40	22	24	1	32	6	2 t.	3	10 t.	None
20	12	20	1	16	4½	1 t.	3	6 t.	5
10-15	6	20	¾	16	3	1 t.	3	2 t.	5
L5					L6				
Band	Freq. Mc.	L µh. (Nom.)	Type	Y1 Mc.	Freq. Mc.	L µh. (Nom.)	Type	C5 pF.	C11 pF.
80	12.75	3.3	21A336	7.5	7.5	6.8	21A686	45	25
40	16.25	2.2	21A226	11.0	11.0	3.3	21A336	30	20
20	23.25	1.5	21A156	18.0	18.0	2.2	21A226	20	10
15	30.25	1	20A106	25.0	25.0	1.5	21A156	None	None
10	37.5	0.82	20A827	32.00 33.50	32.25	1	20A106	None	None
	38.5	0.82	20A827	33.0 33.5	33.25	1	20A106	None	None
L7 — 8 turns No. 20, 1 inch diam., 16 t.p.i.									

L1/L2 and L3/L4 (as well as L7) are of Miniductor, Air Dux, or Polycoll stock, with the indicated number of turns removed to provide spacing between the main coils and the coupling links.

L5 and L6 are iron-slug coils (phenolic). Type numbers are J. W. Miller (suffix RBI). Those with prefix 20 are ¼ inch diam.; prefix 21 indicates ¾ inch diam.

solidly in place by soldering the shield to conveniently located soldering lugs along the way. Shielded wire should also be used for all a.f. grid leads to avoid unpleasant feedback problems. R.f. by-pass capacitor leads should be as short as possible, using the centre post of the related tube socket as a common grounding point.

TESTING THE V.F.O. AND B.F.O.

The v.f.o. tuning range should be checked first with all tubes except the v.f.o. voltage regulator tube out of their sockets. After power has been turned on and the v.f.o. allowed to warm up a v.t.v.m. with an r.f. probe should show about 2 volts at the output coupling capacitor.

The v.f.o. frequency can be checked by comparing it with the signal from a calibrated source, such as a BC-221 frequency meter, or a general coverage receiver. Set C8 at about midpoint. Set the tuning capacitor C6 at about 3 degrees from maximum capacitance. Then adjust C7 to bring the frequency to 5.0 Mc. Turn C6 to about 3 degrees from minimum capacitance, and check the frequency again. If the frequency is higher than 5.5 Mc., spread the end turns of the coil apart, and repeat the process. If the frequency is too low, squeeze a few of the turns slightly closer together, and repeat the process. It should be possible to arrive at an adjustment where the 5 to 5.5 Mc. band occupies about 95 per cent. of the dial, with the band central on the dial.

Plug in the b.f.o. tube and check the r.f. output voltage. It should be about the same as from the v.f.o., i.e. 2 volts.

CHECKING THE AUDIO SECTION

Plug in the audio tubes. With speaker or headphones connected, and the a.f. gain control near maximum, a sharp click, when the top end of the gain control is touched with the lead of a pencil, will tell you that the audio stages are working.

I.F. ALIGNMENT

Plug in the 7360 mixer and i.f. tubes. Connect the r.f. probe at the arm of S4B. Introduce a 9 Mc. signal at the input to the last i.f. stage. The author used the crystal calibrator as the source, with a 9 Mc. crystal, borrowed from his s.s.b. exciter, plugged into the calibra-

tor. The 20 pF. calibrator coupling capacitor was temporarily disconnected from pin 1 of the 6AZ8, and connected by means of an extension lead to pin 1 of the last 6BA6 i.f. tube. (A reasonably accurately calibrated r.f. signal generator may be used, if available.) Tune T5 for maximum output. Move the signal source to pin 1 of the second i.f. tube, and adjust T4. Do the same with the first i.f. tube and T3. You will probably have to reduce the i.f. gain as you move down the i.f. strip to avoid burning out the diode in the probe.

Introduce the signal at the output connection of the crystal filter, and adjust T2. Finally, inject the signal at pin 3 of the 7360 mixer, and adjust T1. (If you are using an r.f. signal generator, you may have to jockey the frequency slightly to hit the centre of the crystal filter passband.) Reconnect the calibrator coupling capacitor to the plate of the 6AZ8.

S METER ADJUSTMENT

The next step is to adjust the S meter circuit, since it will be used in adjusting the preselector. With V4 out of its socket, adjust R6 for full-scale S meter reading. Plug in V4. Allow the tube to warm up and, with the a.g.c. switch off, adjust R5 for a zero reading.


HETERODYNE TUNING

Now plug in the 6KE8, and adjust each slug-tuned coil (L6) for approximately 3 to 4 volts as measured with the r.f. probe at the "hot" end of the coil. The lower frequency crystals are capable of producing much more than 4 volts; the higher frequency crystals may not provide quite 4 volts. Tune for all you can get up to a maximum of 4 volts.

Using a grid dip oscillator, tune the heterodyne mixer coils (L5) to the frequencies listed in the coil table. Be sure that the band switch is set to the band corresponding to the coil you are checking, because the stray capacitance may vary with the switch position.

PRESELECTOR ALIGNMENT

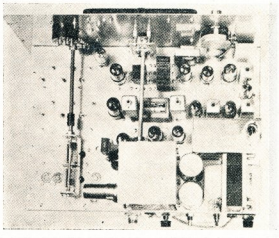Alignment of the preselector coils can now be undertaken. The author



built the preselector coils for 80 metres first, and aligned the front end on this band before proceeding to the higher frequency bands, in order. However, it need not be done this way. The alignment procedure is the same for all bands. The important consideration in making the coils is to keep L2 and L4 as nearly identical as possible, including lead length and proximity to chassis and shields.

With a set of coils in place, introduce a signal near band centre at the antenna connector. Set the v.f.o. to mid scale, and the mode switch to one of the side-band positions. Adjust C2, and the slug of L5 for maximum S meter reading. Then tune the preselector slowly across the signal. If the signal peaks at two dial settings, it means that the circuits are not tracking. By cautious adjustment of C1, and the turn spacing of either L2 or L4, a condition should be found where only a single S meter peak occurs as C2 is tuned across the signal. (The paragraphs on r.f. alignment in the "Receiving Systems" chapter of the A.R.R.L. Handbook explain how this is done.)

TEMPERATURE COMPENSATION

To adjust the v.f.o. temperature compensation, the most stable frequency source you can get is required. The crystal calibrator will do nicely. Allow the receiver to warm up thoroughly; leave it on for at least an hour or two. Tune the receiver to zero beat with the calibrator. Then, as drift occurs,

adjust C8 slightly, and bring the receiver back to zero beat with C7. Continue to do this until no drift is apparent.

B.F.O. ADJUSTMENT

Remove the cover of the b.f.o. enclosure, and adjust trimmers C12 and C13 for optimum s.s.b. reception. Most 80 and 40 metre stations use L.s.b., while those operating in the higher bands use u.s.b. (Most c.w. operators prefer the u.s.b. position.) The b.f.o. frequency is adjusted so that it falls only high enough on the filter slope to assure adequate low frequency response. With this adjustment, the "other side" of a c.w. signal simply is not there.

V.F.O. CALIBRATION

After checking to make sure that the 5 to 5.5 Mc. band is still centred on the dial, the dial may be calibrated (0 to 500, and 500 to 0) against a standard, such as a BC-221 frequency meter. The tuning should be found to be close to linear. A single dial calibration for all bands requires the exact crystal frequencies listed in the Table. Crystals not too far off on the high side can be "rubbered in" with a small compression trimmer in parallel with the crystal. Crystals on the low side must be ground or etched in. (The 3.5 Mc. band edge marker will provide a reference.) Otherwise, C7 in the v.f.o. will have to be retrimmed each time bands are changed, zeroing the v.f.o. against the

calibrator with the v.f.o. dial set at the previously calibrated zero mark.

Before placing the receiver in the cabinet, punch four or five holes through the bottom, and along the top back of the cabinet for air circulation. You should now be able to make R5 copy of signals that your Amateur friend down the block may not be able to hear. Congratulations!



PROVISIONAL SUNSPOT NUMBERS

SEPTEMBER 1968

Dependent on observations at Zurich Observatory and its stations in Locarno and Arosa.

Day	R	Day	R
1	78	16	79
2	82	17	81
3	139	18	86
4	131	19	89
5	128	20	91
6	96	21	95
7	98	22	107
8	106	23	129
9	128	24	153
10	138	25	197
11	145	26	198
12	150	27	183
13	163	28	149
14	113	29	137
15	88	30	91

Mean equals 120.7.

Smoothed Mean for March 1968: 104.8.

Predictions of the Smoothed Monthly Sunspot Numbers

October	106	January	100
November	104	February	98
December	102	March	97













—Swiss Federal Observatory, Zurich.

AMATEUR FREQUENCIES:

USE THEM OR LOSE THEM!


PREDICTION CHARTS FOR MARCH 1969

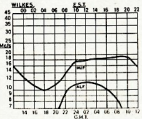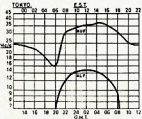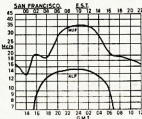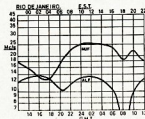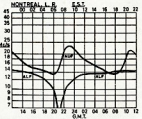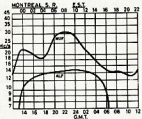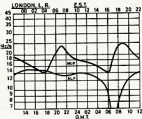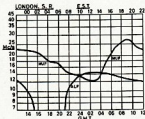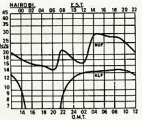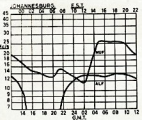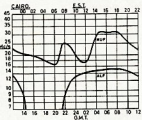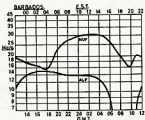(Prediction Charts by courtesy of Ionospheric Prediction Service)



New Equipment


VERSATILE AC BRIDGE

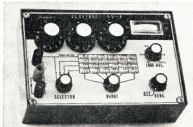

Model BR8 AC Bridge branded "Rapar," measures resistance, capacitance, inductance and transformer turns ratios with high accuracy performance. The unit operates from 9-volt battery; dimensions: 7½" wide x 5" deep x 3" high. Housed in blue hammettore finish metal case; price: \$46 plus 15% sales tax.

Further information from Radio Parts Pty. Ltd., 562 Spencer St., Melbourne, Vic., 3000, and City and East Malvern branches.

LOG PERIODIC FOR 6-2 METRES

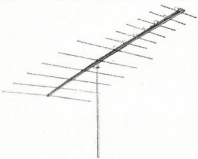

Shortly available from Bail Electronic Services is a log periodic antenna for 6 and 2 metres. Manufactured by Hy-Gain Electronics Corp., U.S.A., this model LP62 antenna is claimed to provide the ultimate in uni-directional, duo-band performance on 6 and 2 m. All elements and boom are constructed of heavy seamless aluminium tubing. Designed to feed from 52 ohm co-ax.

Electrical Specifications: gain (6 mx), 8 db; gain (2 mx), 15 db.; front-to-back ratio, 25 db.; max. power input, 1 kw.; v.s.w.r., less than 2:1; impedance, 52 ohms; unidirectional pattern.

Mechanical Specifications: Longest element, 9 ft.; boom length, 24 ft.; turning radius, 16 ft.; net weight, 20 lbs.; max. wind survival, 100 m.p.h.; mast diameter, 1½" o.d.

Further details from Bail Electronic Services, 60 Shannon St., Box Hill North, Vic., 3129; or from N.S.W. rep., Sandy Bruce-Smith, 47 Hyman St., Tamworth, N.S.W., 2340.

PANORAMIC DISPLAY UNIT




Designed as a companion unit to the Eddystone 830/2 communications receiver (also illustrated), the EP20 panoramic display unit now available is intended for applications where a visual display of h.f. or i.f. signals is advantageous. Characteristics such as modulation, amplitude, presence or absence of spurious emissions and interference, may be observed at a glance.

The EP20 is particularly useful when setting up a receiver for s.s.b. or f.s.k. signals. An additional facility is that the display unit can be used as a wobbulator for the visual alignment of the i.f. stages of receivers.

Specifications and other details obtainable from R. H. Cunningham Pty. Ltd., 608 Collins St., Melbourne, Vic., 3000.

MOTORISED ANTENNA ROTATOR

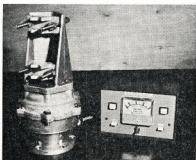

Heavy duty antenna rotator, "Emota-tor" model 1100M, available shortly from Japan, features heavy cast aluminium construction, stainless steel bolts, nuts and washers. Bearing design with 90- ball bearings provides high vertical carrying capacity enabling it to withstand bending pressures due to unbalanced weight, wind, etc. Limit switches prevent over-run. Positive braking with solenoid operated double plunger. Drive is through steel gears from a fractional horse power motor.

Specifications: Torque, 400 kg./cm.; vertical moment, up to 7,000 kg./cm.; time for one rev., 55 secs. (approx.); brake power, 5,000 kg./cm.; supports beam assembly weight of 200 kg.; max. vertical thrust, 1,000 kg.; mast diameter, 1½" to 2½"; weight, 17½ lb. (approx.); control cable, 7 wires; approx. sizes,

13½" high, 5½" base diam., 7½" largest diam.

The Indicator-Control Box is attractively finished in grey lacquer with large illuminated meter, indicator lights and piano lever "left-right" controls coupled to micro-switches. Transformer is contained within the control box. Size: 5½" x 8½" x 4". Weight, 5 lb. 12 oz.

Further information from Bail Electronic Services, 60 Shannon St., Box Hill North, Vic., 3129.



FEDERAL AWARDS

W.I.A. & Mc. W.A.S.

Additional members to 31/12/68—

Cert. No.	Call	Additional Countries
83	VK4ZRG	2
84	VK3AQR	2

Intending applicants for this award are reminded that new rules are now in effect in relation to the number of VK call areas required. Full details will be found in "A.R." June 1968, p. 14.

AUSTRALIAN D.X.C.C. COUNTRIES LIST OMISSION

Despite numerous checks to ensure accuracy, U.N. Turkmenistan was omitted in the list as published in January 1969 "A.R."

It is suggested that D.X.C.C. members and others interested in the list should insert the addition in the space below UL7, Kazakh, at the foot of column three.

Any inconvenience caused to members by this omission is regretted.

FEDERAL AWARDS MANAGER—CHANGE OF ADDRESS TO WHICH APPLICATIONS FOR AWARDS ARE TO BE SENT

In future all applications for Awards, enquiries, etc., should be addressed to—

Federal Awards Manager, W.I.A.,
P.O. Box 67,
East Melbourne,
Victoria, 3002,
Australia.

"ELECTRONICS AUSTRALIA" D.X.C.C. LISTING

Amateurs are advised that the D.X.C.C. Countries List, as published in "Electronics Australia," December 1968, Amateur Band News and Notes, pages 156 and 157, is NOT the current list for the D.X.C.C. Award. This list was taken from that published in "A.R." in January 1968 and since that time several important changes have taken place. The only official up-to-date list is that published in "A.R." January 1969.

—Geoff Wilson, VK3AMK,
Federal Awards Manager.

W.I.C.E.N. EXERCISE BY VK3 NORTH-WESTERN ZONE

A very successful civil defence exercise was held at Mildura on Sunday and Monday, 26th and 27th January, by the North Western Zone members. V.h.f. communication was provided for a 37½ mile Murray River Marathon Swim.

The problem of providing reliable v.h.f. communication can be appreciated when it is remembered that the actual river level is much lower than the surrounding country, added to this are cliffs and heavily timbered areas. Channel B 146 Mc. was used throughout, and all equipment being MR3A units.

A houseboat accompanying the eleven swimmers was fitted with a ground plane antenna, and from the start of the race at 1100 Saturday to 1730 Sunday, communication to the Mildura Base was through a portable station located on the cliffs at Mindook Station, approx. 17 air miles from Mildura. At 1730 Sunday a mobile station was brought into use to cover the houseboat, while the portable station shifted from Mindook to Monak. The Monak location was used from 2000 hours to 0230, at this stage the base was working direct to the houseboat for some time. The marine/mobile operation ceased at 0600 Monday morning when the first swimmer arrived at Mildura, and from then to the arrival of the last swimmer at 2320 Monday, mobile stations were used to pass information from the swimmers' locations to base. The arrival of the swimmers were handled, dozens of which were phoned from the base to their destination.

NEW CALL SIGNS

SEPTEMBER 1968

[Although the following list was issued by the F.M.D. Dept. under the date of September 1968, all the VK3 call signs cover from June to September 1968.—Ed.]

VK1DI—D. I. Ralph, Flat 7, Clayton Court, Carroll St., Hughes, 2605.
 VK1ZDR—R. C. Speer, Lawley House, Barton.
 VK1ZJM—J. A. Mowatt, Station: Reid House, Allara St., Canberra, 2609; Postal: 4 Hinemok St., Pannania, 2213.
 VK2AD/T—A. J. Bruce-Smith, 47 Hyman St., Tamworth, 2340.
 VK2HI—A. H. B. Brodick, 18 Rhoda Ave., Wagga Wagga, 2650.
 VK2NM—L. Pollack, 2/241 Forest Rd., Arncliffe, 2205.
 VK2QN—E. C. Roberts, 588 Punchbowl Rd., Lakemba, 2195.
 VK3AD—C. McKelvie, 19 Harley Rd., North Avalon, 2107.
 VK3BPB—P. Bass, 83 Nicholson St., Strathfield, 2135.
 VK3ZFF—F. F. Teixeira, 17/70 Arthur St., Randwick, 2031.
 VK3ZGP—G. K. Facey, 13 Coral Rd., Cronulla, 2230.
 VK3ZHI—H. A. Tyrer, Lot 4, Kingsford Pde., Macquarie Fields, 2564.
 VK3ER—Eastern & Mountain District Radio Club, 426 Riverside Rd., Surrey Hills, 3127.
 VK3HV—P. J. Trutmann, 7 Nerita Gardens, Corio, 3214.
 VK3JD—J. G. Ditchburn, 80 Clausen St., North Geelong, 3068.
 VK3NS—J. A. Taylor, 2 Valerie St., East Bentleigh, 3165.
 VK3UI—J. Van Elkkan, 520 Glenferrie Rd., Hawthorn, 3122.
 VK3VN—D. A. Sinclair, 208 Canterbury Rd., Canterbury, 3106.
 VK3VR—J. H. Dexter, 15 Glenish Lane, Mt. Eliza, 3930.
 VK3WP—A. B. Endersbee, 169 Canterbury Rd., Canterbury, 3130.
 VK3YC—J. Douglas, 4 Brodie St., Bendigo, 3550.
 VK3AFL—D. A. Page, 152 East Boundary Rd., North Melbourne, 3105.
 VK3ALA—S. C. McLean, 204 Balclutha Rd., Caulfield, 3162.
 VK3AIC—A. Nedeck, 19 Talofa Ave., Ringwood East, 3135.
 VK3AMW—Wangaratta and District Amateur Radio Club, 5 Gayer Ave., Wangaratta, 3670.
 VK3AOR—R. W. McLean, 313 Crompton St., Ballarat, 3350.
 VK3AQ—J. McL. Bennett, 56 Lancaster St., Ormond Estate, 3163.
 VK3ATP—J. B. B. White, Grant St., Point Lonsdale, 3223.
 VK3ATO—Wireless Institute of Aust., Midland Division, 540 McIvor Rd., Bendigo, 3550.
 VK3AUT—A. U. Magnus, 10 Hillcrest Rd., Glen Waverley, 3146.
 VK3AVI—E. H. Connery, 75 South Cres., Northcote, 3070.
 VK3AY—L. Linden, 135 Hume St., Wodonga, 3690.
 VK3AYE—A. Ball, 52 Shells Toe, Casterton, 3311.
 VK3AYV—Rayson, 1588 Dandenong Rd., Huntingdale, 3166.
 VK3AYK—K. F. Price, 1 Valdeira Crt., Heathmont, 3135.
 VK3AZP—R. C. Gilson, Flat 1, 76 Roberts Ave., Springvale North, 3171.
 VK3AZH—K. J. Horstall, Flat 14, 51 Buckley St., Essendon, 3060.
 VK3ZEP—H. F. Paton, Station: 49 Havelock Rd., Hawthorn, 3123; Postal: C/o 18 Selwyn St., Hawthorn, 3123.
 VK3ZHL—C. W. Gliddon, 9 Gloria Ave., Dandenong, 3187.
 VK3ZIU—J. Marks, 13 Melosa Ave., East Brighton, 3187.
 VK3ZIV—J. C. Vandell, Flat 2, 28 Donna Buang St., Camberwell, 3124.
 VK3ZO—E. G. Briggs, 663 Neerim Rd., Hughesdale, 3166.
 VK3ZKI—J. Skimin, 15 Normanby St., Prahran, 3181.
 VK3ZKO—R. J. Broughton, Flat 1, 32 Wattle Rd., Aradale, 3143.
 VK3ZLG—R. J. Green, 22 Shackleton St., Belmont, 3216.
 VK3ZML—L. W. Cerchi, Unit 2, 428 Riversdale Rd., East Hawthorn, 3123.
 VK3ZOH—J. R. Hargrave, 74 Haydens Rd., Beaumaris, 3193.
 VK3ZQ—K. M. Lane, 49 Albert St., Ararat, 3377.

VK3ZSL—A. Slarks, 13 Orchard Ave., Oakwood Park, 3175.
 VK3ZSU—D. G. Politakis, 37 Hoptoun Ave., Morwell, 3640.
 VK3ZTN—P. J. Solly, Station: Rainbow, 3424; Postal: P.O. Box 102, Rainbow, 3424.
 VK3ZVN—L. Sawtell, 43 Clyde St., Box Hill, 3129.
 VK3ZXF—R. H. Hudson, 15 Prince Edward Ave., McKinnon, 3204.
 VK3ZXS—H. Smith, 22 York St., Strathmore, 3041.
 VK3ZYI—S. Curtis, 437 Middleborough Rd., Box Hill, 3136.
 VK3ZZR—R. L. Reid, 3 Ellen St., Springvale, 3171.
 VK3ZZT—A. J. M. Scott, 21 McKean St., Box Hill North, 3129.
 VK3ZZU—P. S. D. Edwards, 101 Main St., Blackburn, 3130.
 VK3ZBT—A. F. Raftery, 22 Princess St., Croydon, 3008.
 VK6AO—C. G. Andrews, 14 Curtis Pl., Melbourne, 6156.
 VK6DB—D. F. J. Benck, 18 Omdurman St., Wagnin, 6315.
 VK6HJ—H. M. Smith, Station: 22 Lockwood St., Exmouth, 6707; Postal: P.O. Box 12, Exmouth, 6707.
 VK6JL—J. L. Lewis, 111 Churchill Ave., Subiaco, 6008.
 VK6JT—S. Brown, 92 Acanthus Rd., Riverton, 6155.
 VK6JU—M. G. Burleigh, 147 Gloucester Cres., Safety Bay, 6169.
 VK6LT—L. F. Toussaint, 19 Errinbee St., Riverton, 6155.
 VK6ZEV—G. D. L. Armstrong, Station: Kojonup, 6311; Postal: C/o Radio Station 6WB, Katanning, 6317.
 VK6MR—M. D. A. Richardson, Station: 18 Mary St., Stuart Park, Darwin, 5790; Postal: P.O. Box 228, Darwin, 5794.
 VK8ZA—J. C. McLeannan, 582 Fernau St., Nightingale, 5702.
 VK8ZEC—P. M. Van der Velden, C/o N.T. Musical Pty. Ltd., 34 Cavanagh St., Darwin, 5790.

CANCELLATIONS

VK2GB—W. J. Birdsall, Not renewed.
 VK2IB—H. T. S. Banks, Deceased.
 VK2WZ—J. H. Lean, Not renewed.
 VK3YV—C. A. Coyle, Not renewed.
 VK3AHN—D. J. Murphy, Not renewed.
 VK3AIO—R. A. Emmerton, Not renewed.
 VK3AJO—J. A. Brauer, Now VK6JL/T.
 VK3ZJO—A. H. B. Brodick, Now VK2HI.
 VK3KJ—J. Rich-Phillips, Deceased.
 VK3VJ—W. Adams, Now VK2IL.
 VK3ABQ—J. S. Brown, (Sgt.), Transferred to Western Australia.
 VK3AGS—G. E. Sheeran, Now VK2BGS.
 VK3AIO—W. M. Ryan, Now VK4VR.
 VK3AMR—J. A. Howie, Now VK2AYH.
 VK3AQD—D. K. W. Bradbury, Transferred to New South Wales.
 VK3ZJP—J. A. Taylor, Now VK3NS.
 VK3ZMD—J. F. Davis, Transferred to New South Wales.
 VK3ZMA—M. W. Benzen, Overseas.
 VK3ZQZ—J. McL. Bennett, Now VK3AQP.
 VK3ZVR—S. Rayson, Now VK3AYF.
 VK3ZVZ—R. W. McLean, Now VK3AOR.
 VK3AJ/T—R. A. Hipwell, Transferred to Victoria.
 VK3LV—J. R. Godson, Transferred to Queensland.
 VK3LV—J. R. Godson, Ceased operation.
 VK3ZJK—W. J. McLennan, Now VK2BCA.
 VK3ZJL—P. M. van der Velden, Now VK3ZEC.
 VK3AAN—F. W. Noble, Left country.
 VK3GHI—W. G. Hayman, Deceased.
 VK3GAZ—C. G. Andrews, Now VK6AO.
 VK3ZDN—J. S. Brown, Now VK3AT.
 VK3ZDR—R. C. Speer, Transferred to New South Wales.
 VK3ZJL—F. M. Benck, Now VK6DB.
 VK3ZGL—J. L. Lewis, Now VK6JL.
 VK3ZLT—L. F. Toussaint, Now VK6LT.
 VK3ZOF—W. E. Dixon, Ceased operation.
 VK3ZDE—W. Spaulding, Transferred to New South Wales.
 VK3ZMR—M. D. A. Richardson, Now VK6MR.

GELOSO CALENDAR '69

R. H. Cunningham Pty. Ltd. are making available free on request the Geloso calendar for 1969. Beautifully printed in full color, the calendar shows historic buildings and places in Italy. Requests should be addressed personally to Mr. R. H. Cunningham, 608 Collins Street, Melbourne, Vic., 3000.

THE QUESTIONNAIRE

(Continued from Page 7)

time and then through again, but please, no box Brownie shots or similar. Find a competent photographer (there will be one in your Division) and send us good clear prints, preferably no smaller than 10" x 8", sharply focused, and with reasonably good contrast.

We were surprised at the number of requests for the history of Amateur Radio in Australia. The Federal historian, Mr. George Glover, has been working on this project for several years, collating and checking through old records, and when last contacted on the matter was able to report considerable progress having been made. His writings cover the first fifteen years and in draft form, copies have been sent to many old-timers for comment and additions or corrections that they can recommend. We expect to be making full use of this work in due course.

A common request was for more technical articles. Here we are largely controlled by what we receive, and despite some of the comments, very few are rejected. Over the last five years only ten articles submitted have not been used, one of these because the author has never completed it. From the replies we now know that the articles we have published are: too long, too short, too technical and too simple, give too much detail and too little detail. In other words, we have no hope of winning. We must assume that a magazine published for Amateurs will be read by Amateurs, who by the very virtue of passing written examination to obtain their licence have a certain basic level of knowledge on the subject, and this should be the minimum level to which we publish. On the other hand, we are faced with finding the maximum level, without getting too high for the majority of readers. To this question we have no answer, as there is always a percentage of readers anxious to improve their knowledge of the subject, and this is one of the prime objectives of the W.I.A.

To produce all the articles for which we are asked, we would need a laboratory and a large staff. We now believe there is more than sufficient talent within our own ranks to produce all the material we could ever use and we refer you back to the policy item reproduced earlier in this report.

As a guide to prospective sub-editors, we are looking for articles on equipment for the u.h.f. frequencies. We are now aware that considerable work is being done on 432 and 1296 Mc, but we have not been favoured with any articles.

There will be no report next month, as time will have to be devoted to the annual report for the Federal Convention. With the May issue, we hope to have a look at the frequencies and modes being used, and, space permitting, a survey of a few more of the suggestions received.

Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the Publishers.

DX-PEDITION TO ANDORRA

Editor "A.R.," Dear Sir,
Last season I was active from the principality of Andorra with the call PX1FD. I now intend to re-activate this call about Easter, probably from 15th to 18th April.
During last August last we formed a team with PX1KT and PX1YI. All arrangements are being made for PX1YI to accompany the DX-pedition which will probably be in May. IKT will also be on the air. It could thus be that the station would be operated around the clock.
Further details are not yet determined precisely, but will be known definitely by the end of January/early February. Licenses are being asked for and will probably be granted in due time.
Could you possibly insert a few lines in the next issue of "Amateur Radio" to inform the VK Amateurs about this opportunity.
I shall, of course, keep you posted on all details of frequencies, time scheduling, transmitters used, etc.,
Thanking you beforehand for your collaboration, I hope you can avail yourselves to make many solid QSOs between VK and PX.
My best 73 in the meantime.
—Guy Gillian, ON5FD.

1200 Mc. TESTS

Editor "A.R.," Dear Sir,
I wish to advise you of recent experiments which have been carried out on 1200 Mc. band. On Sunday, 28th December, 1968, during the New Year's Field Day Contest, while portable at Moorabbin, near Bowral, I contacted VK3ZAH at Hornsby—a distance of 65 air miles. The portable gear used consisted of completely home-made equipment, running from a transistor power supply with 9 watts output at 1200 Mc. from a varactor; receiving equipment consisting of a crystal locked converter into a tunable antenna. The antenna was a twin 10-turn helix a wavelength apart, with a solid metal reflector.
The gear at Barry's end (VK3ZAH) was running on a 2000 Mc. transmitter, a 4 ft. dish, crystal locked converter to an ART. Signal reports exchanged were 5 and 6 and 5 and 5. A very good contact, which prompted us to try it again. The following morning, during week-end, so on Sunday, 5th January, 1969, when we proceeded to a mountain, 135 road miles from Sydney, we found it was possible to work Bill VK3ZAC over a path of 71 air miles from Shooter's Hill to Narwee. Signal reports were 4 and 5 and 5 and 6, the portable gear being the same as used in working Barry. Bill used a varactor multiplier with seven watts output to a quad helix with a crystal locked converter to BC244.
Both these contacts have been confirmed and distances have been agreed upon by both parties.
—R. C. F. Norman, VK3ZCF.

FOREIGN STATIONS AND N.F.D. CONTEST

Editor "A.R.," Dear Sir,
I would be obliged if you would find space in "A.R." to print the following, which I see as a constructive statement to the notice of members a ridiculous situation that has developed in respect of the Memorial to the late Mr. Moyle, whom I held in the highest regard.
I have read in the columns of "A.R." various letters pertaining to the N.F.D. Contest, those for and against its coincidence with the A.R.R.L. Contest. Insofar as they conflict, these worthy letters are relevant. They do, however, miss the wood for the trees.
All those stations that worked foreign stations and included these stations in their scores must be aware of the inequality themselves. Whether it transpires that this is formally or not under the rules as they stand, these worthy stations were outside the Contest and were at a disadvantage over other rule-abiding stations.
The Objects of the Contest make it clear that VK stations are to work VK stations, only.
The Objects say: "The operators of Portable and Mobile Stations within all VK Call Areas will endeavour to contact other Portable and Mobile Stations in Australia and Overseas Call Areas."
Rule 6 defines a Call Area. Rule 8: "The following shall constitute Call Areas—VK1,

VK2, VK3, VK4, VK5, VK6, VK7, VK8, VK9 and VK10.
Under the Rules there is no place for a G3 call area or a W6 call area, etc. Where the Objects speak of "Overseas Call Areas" they clearly refer to those Call Areas being VK Call Areas without Australia, i.e. not being within Australia proper, e.g. Willis Is., Papua, etc.

One could quote analogy after analogy from life where self interest conflicts with the social mores and social values as laid down in various Statutes, Ordinances, Orders, Rules, etc., but the fact of the matter remains the same, a Rule, etc., is either observed as it is laid down or it has not been.
Any discussion that comes later will come after the fact that the rules of the contest have been blatantly broken, mostly by ignorance and constant reading of the Rules, it is hoped, but nevertheless broken.

It is now up to the Contest Committee to decide what to do, and the best of luck to them, because whatever it is, will it be popular with everyone?
—R. F. Meaney, VK3HA.

"CQ" SSB AWARD RULES

The 2 x SSB Certificate will be issued to any licensed amateur station in proof of contact with 100, 200 and 300 countries. Stickers will be issued for each additional 25 countries confirmed up to 300, thereafter they will be issued in increments of 25. The form shall consist of a proper QSL card to be checked by the 2 x SSB Award Manager or by one authorized check-point operator of the DX Awards. (W.I.A. Awards Manager in VK.)

1. All applications should be submitted on official application form "CQ1007. This form can be obtained free by sending a self addressed stamped envelope to the 2 x SSB Award Manager.
2. All QSL cards must be clearly marked 2 x SSB, and be in alphabetical order.
3. Claims for 100 countries must be included in the first application.
4. Confirmations must be accompanied by a list of claimed countries and stations to aid in checking and for future reference.
5. Include with the application eight IRCs to defray cost of the certificate. Sufficient postage for the return of confirmations must be included with a self addressed stamped envelope with each application. When sending for endorsements, two IRCs or a self addressed stamped envelope should accompany each application.
6. All contacts must be with licensed land based Amateur stations working in authorised Amateur bands.
7. All contacts submitted by applicant must be within a 250-mile radius of the original location.
8. Any altered or forged confirmations will result in permanent disqualification of the applicant.
9. Fair play and good sportsmanship in operating are required of all Amateurs working towards 2 x SSB Award. Conscious use of poor ethics will result in disqualification.
10. Once a country has lost its status as such, it will automatically be deleted from our records. There will only be current country count.

11. Decisions of the "CQ" DX Awards Advisory Committee on any matter pertaining to the administration of this award shall be final.
12. All applications should be sent to: Louise Rippe, WHBDB, 2 x SSB Award Manager, 3785 Susanna Dr., Cincinnati, Ohio, U.S.A., 45239.
VK applicants should forward their QSLs and check-lists to W.I.A. Awards Manager, who will certify applications and return cards. (Reproduced by permission of the DX Editor "CQ" Magazine).

CONTEST CALENDAR

- 1st/2nd Mar: 35th A.R.R.L. DX Test (Phone Section).
- 1st/16th Mar: I.A.R.C. C.W./R.T.T.Y. Contest.
- 8th/9th Apr: 32nd B.E.R.U. Contest (R.S.G.B. C.W.).
- 15th/16th Mar: 35th A.R.R.L. DX Test (C.W. Section).
- 29th Mar/1st Apr: I.A.R.C. Phone Contest.
- 5th/6th Apr: Polish DX C.W. Contest.
- 12th/13th Apr: "CQ" W.W. WPX. S.S.B.
- 19th/20th Apr: Helvetia 23 Contest.
- 26th/27th Apr: P.A.C.C. C.W./Phone Contest.
- 28th/29th Oct: "CQ" W.W. DX Contest—Phone Section.
- 29th/30th Nov: "CQ" W.W. DX Contest—C.W. Section.

—D. Rankin, F.E.

1969 I.A.R.C. PROPAGATION RESEARCH COMPETITION

(A DX CONTEST WITH A PURPOSE)

RULES

Contest periods: This year, the contest will be run in two sections. C.W./RTTY from 0001 GMT, 1st March, to 2400 GMT, 16th March. Phone from 0901 GMT, 29th March, to 2400 GMT, 13th April.

Objective: The objective remains the same. Work as many stations in as many different Call Zones as possible. Countries, do not count in the score. Work your own Zone only once for Zone credit.

Bands: All bands—1.7 through 30 Mc.

Exchange: RS or RST report plus your C.P.R. Zone number.

Duplicate QSOs: You may work the same station as often and for as long as you wish. When a single QSO exceeds 6 minutes, a new log entry shall be made for each 6 minutes or part thereof.

Logging: Use GMT only. Observe rule for duplicate QSOs. QSO may be made in another contest or with a station not participating in this test, provided all necessary information is logged.

Scoring: One point for each QSO except no contact credit for working stations in your own Zone. Objective: Multiplication of one for each Zone on each band. You may work one station in your own Zone for Zone multiple only. Total score is the sum of all contacts multiplied by the total Zones for all bands.

Entry Classes: Entries will be accepted in the following categories:

- Single Operator—Single Band.
- Single Operator—All Bands.
- Multi-operator—All Bands.
- Radioteletype—All Bands.
- Mobile—All Bands (includes all categories of mobile).

All Events—This is a new category. You may submit a total score for all modes and bands.

Awards: Winners in each category in each Zone will receive a suitable certificate or other award. All entries of 100 or more valid QSOs will receive a CPR Certificate of the appropriate grade.

Logs and summary sheets may be obtained from I.A.R.C. Box 8, 1211 Geneva 20, Switzerland, or from the Chairman of the Contest Committee. Send all logs to the following addresses unless otherwise instructed. Logs must be posted prior to 1st June, 1969.

L. M. Rundlett, Chairman,
I.A.R.C. Contest Committee,
200 Eye Street, N.W.,
Washington, D.C. 20006.

— D. —

"CQ" WORLD WIDE WPX SSB CONTEST, 1969

PRECIS OF RULES

Time: 0000 GMT, 12th April, until 2400 GMT, 13th April.

Single operators can only work a maximum of 25 stations within the above stated 48 hours. The 18 hours of non-operating time must be shown in the log and may be taken in up to five periods during the contest. Multi-operator stations can operate the full 48 hours.

Bands and Mode: 3.5 Mc. to 28 Mc. S.S.B. only.

Exchanges: 59001, 59002, etc.

Scoring: Three points per contact with stations on different continents. One point per contact with stations on the same continent. No points are allowed for contacts with stations in the same country but are permitted for multiplier purposes.

Multipier: Sum of the number of prefixes worked multiplied by the number of contact points. N.B.—A prefix may be counted only once during the contest irrespective of the band worked. W2, WA2, KA2 are different prefixes.

Log: To "CQ" WPX Contest Committee, 18 Vandewater Ave., Port Washington, N.Y., 11050, U.S.A.

N.B.—Full details appear in March "CQ" magazine and serious contestants are recommended to read these details.

ASCAU—Box 200, Francistown, Botswana.
 VR7JE—Box 2, I.L.E., Zambesia, Mozambique.
 CR8AL—L. Fernandes, Dill, Portuguese Timor.
 CT1AK—Box 143, Ponta Delgada, S. Miguel.
 DX1NY—B. Smith (K4NY), C/o. S.E.A.C.R.,
 A.P.O., S.F., 96274.
 ZS2MI—Box 538, Germiston, S. Africa.
 KV4CI—direct only—J. Miller, Box 1853, St.
 Thomas, Virgin I.

ACTIVITIES

180 metres often open to DX regions according to George L6042. He has been hearing the following: KJ2CN 1801 kc. 11422, W6QHG 1992 kc. 14205, JAGNLC 1801 kc. 1506. George says the "Condition" right at the button. On the Jan. 11 Trans-Pacific Test, Heard W5HPC, W8ANO, W6QDG (1579), WABGO, KJ2CN, W8KRW, and some weaker ones. KJ2CN and WABGO continuously called VK5KO, who apparently had a good signal over there, but John didn't hear them. (Thanks George.) Further reports of good good 20 m. have been come from Fred VK4RF. A large list of 63 call signs worked (a.s.b.), every single one a winner, bears this out. Unfortunately space does not allow publication of the whole list, but a few picked at random are 5A7X, 7Q7AM, 7U7AJ, 7J1AJ and 7P2CY. Clearly now the time for 20 metres. (Thanks Fred.)

THE XL OPERATOR CLUB

The membership of this fraternity is based on the "long term service and excellent achievements in the field of Amateur Radio. The requirements are intensive activity over many years on various bands and

A minimum of 40 points is required for membership. The points may be earned as follows:

- (1) Five points for the first full 10 years the applicant has been licensed, PLUS three points for each five years thereafter.
- (2) Five points for each 20 DXCC countries confirmed, PLUS three points for each additional 50 countries confirmed.
- (3) Five points for each 100 DXCC countries confirmed on EACH of the 20, 21 and 14 Mc. bands.
- (4) Three points for each 50 DXCC countries confirmed on EACH of the 50 and 6 Mc. bands.
- (5) Two points for each 20 DXCC countries confirmed on EACH of 1.8 Mc. and v.h.f./u.h.f. (v.h.f./u.h.f. is defined as 1.8 Mc. and above).

The country totals are calculated regardless of the mode of operation. A.R.R.L. DXCC rules apply for counting the countries. If you can claim at least 40 points, send your application to Award Hunters' Club International, C/o. OH2YV, J. Velamo, Isokari 4-B-30, Helsinki, Finland, for full details. (Note: The dress, plus (1) the date of your first transmitting licence, (2) the DXCC score confirmed (or credited by A.R.R.L.), (3) number of countries confirmed, and finally, certify personally that the information presented is true. No other certification is necessary; the word of XL operators is trusted. If false information is given, it will spoil the Ham Spirit. Enclose sufficient return postage (there is no membership fee.)

WORLD WIDE POLL OF MOST WANTED COUNTRIES

Readers are requested to send to G. Watts, 62 Belmont Road, Weymouth, 27-T-2, U.K., a list of "most needed" countries (no more than 25). As G. Watts bulletin "DX News" is read by most of the world's top DXers, the results will be published in the next DX-pedition. The results will be published in this column as soon as they come to hand, and the country's popularity will be indicated, providing valuable information for those making DX-peditions. It is in the interest of all readers to participate in this Poll. (Anyone wanting to save postage can send their list to me and I will airmail it to G. Watts.)

SUMMARY

More activity reports are needed. It is a pity that out of so many readers only two can be bothered sending in reports. Surely there are others who have had interesting experiences on the air that others would like to hear about. How about it, chaps? Acknowledgements to DX News, LIDXA, ZL2AFZ, VK3VZ, OH2YV, VK4RF and GCHHT. 73, Peter VK3APN.

FAIRCHILD APPOINTMENTS

Recent additions to Fairchild Australia Pty. Ltd. sales engineer force include Robert C. Hunt who will assist Phil Cohen in Melbourne, and Brian Shirley in Sydney who will assist David Finch.

Sub-Editor: CYRIL MAUDE, VK3ZCK
 2 Clarendon St., Avondale Heights, Vic., 3034

Another summer season is almost over and the DX reports are very poor. Judging by the numbers exchanged by those taking part in the Ross Hull Memorial V.H.F. Contest and the poor DX conditions this year's scoring will be one of the lowest on record.

We would appreciate news from all other States for this page in "A.R." but please keep it to material that is of interest to all readers and not of local gossip that is out of date by the time I receive it. Closing dates for copy for the V.H.f. page of "A.R." for the next few months are: May issue, 28th March; June issue 30th April; July issue, 30th May.

73 until next month, Cyril VK3ZCK.

V.H.F. BEACON TRANSMITTERS

- GB3CT—Crownwall, England—144.10 Mc.
- SM4MPI—Sweden—145.96 Mc.
- ZL5AA—Cook Island—622 Mc.
- ZE1JZA—Rhodesy—432.048, 144.016 Mc. 144.0
- JA4, 6, 8, 9GY—50.50 Mc.
- VK5VF—53.00 Mc.
- VK4VF—52.06, 144.193, 432.59 Mc.
- VK3 ATVO—51.76 Mc.
- GH1MB—Malta—70.10 Mc.
- EA4VY—Gibraltar—144.00 Mc.
- ZD7WR—St. Helena—25.992 Mc.
- JA1HGY—51.99 Mc.
- VK3VY—51.44 Mc.
- VK7VF—Devonport—144.90 Mc.
- VK6BF—(1)—Albany—144.50 Mc.
- VK4 TVQ—51.74 Mc.

These beacon frequencies were compiled from data supplied by George VK3ASV, ex VK3ZCG and VK3ZCK.

Any information regarding these or any other beacons that you may know of will be gratefully received and acknowledged in this column.

VICTORIA

The DX hounds on both 6 and 2 metres have had a big set-back over the past few months. Early in December conditions started very dry, and the weather in the States and a few JAs, but also, came Christmas and the New Year, the Ross Hull Contest and little or no rain.

Since then 2 m. has improved a little, but DX on 6 is very sporadic. The majority of openings in the 52-54 Mc. band appear to be in the mornings, early in the afternoon and again in the evening when it is almost impossible for most Melbourne chaps to fire up on 6 m.

An interesting point on the modes used, a.s.b. is on the increase with a large number of VK3s, 6s and 6s using this mode. Here in VK3 there are only a couple of Amateurs regularly using a.s.b. on this band.

Wide and narrow band 7.m. is becoming popular on 6 m. especially in areas where v.h. channel 0 is in use. The net frequencies in most common use are the International 6 m. fm. net on 32.25 Mc. and 52.55 Mc., both of which are vertically polarised.

Band reports: 6 m. is generally poor, but for DX hunters and those not pestered by VK3s and Indians, the evenings can be quite interesting.

2 m. is improving with DX to northern and central VK3, southern VK2, VK5 (Mt. Gambier and Adelaide), and to northern Tasmania. Most of these openings are at night.

Reports have been received of stations in the Melbourne and Geelong areas having heard some ZLs at fair to good strength, but also no ZLs have been reported.

70 centimeters reports suggest that this band is superior to 2 m. Several stations now operate mobile with a single cloverleaf for the radiator and QSO30, 20 tripler as the transmitter, the exciter being the 2 m. mobile rig. This band is also becoming popular on field days.

Many new call signs have been heard on this band lately, but there still appear to be a shortage of receiving converters, judging by the number of cross band contacts being made. DX has been reported from VK1, VK3, VK3 and inland VK3s.

Fox Hunts.—Visitors to VK3 and those in VK3, the regular Fox Hunt night has been changed to the fourth Friday in each month of the year, the last Wednesday, 73, Robert VK3AUR.

Sub-Editor: PETER NESBITT, VK3APN
 32 The Grange, East Malvern, Vic., 3145
 (All times in GMT)

ASSORTED

Steve VK8CC announces that he hopes to visit St. Brandon and Rodriguez Is. some time during the period March to May, but he returns to Europe on vacation. Cali signs will be VQ8CCB (St. Brandon) and VQ8CCR (Rodriguez). 180 through 10 metre operation is planned with particular attention to be given to the I.F. bands to help those who are trying for SBDXCC. QSL direct to Box 14, Curepete, Mauritius. Three IRCs are required for an airmail reply, otherwise cards will go via the Bureau.

Rumors are brewing for an early March DX-pedition to Cocos Is. (TIB), by T12RE, GMB, CF, 4JP and maybe some WS.

VR7CT is QRV Tuesdays: 1st Tuesday in each month on 21060 e.s.b. from 2130z onwards, other Tuesdays 21350 a.s.b. from 2200z. For a sked wire in advance to W6LQZ, Box 261, Grapevine, Texas, 76051. State which you wish to be on freq. Wait for Tom to call you.

ZL5AA/J. Ian ZL5AA has arrived at Campbell Is. where he hopes to operate for two or three months.

It is alleged that French licensing authorities have refused to license for operation from Clipperton Is. While on the topic, W1MQT (who is not QSL manager for TASAB) says that Frank, the operator, is to be replaced by someone from Ismir. He says that the Govt. of Turkey does not permit American personnel to operate Amateur stations there. (DX News.)

All is not lost, however. A.R.R.L. has advised DJ1QP that DXCC credit will now be granted on the cards of his recent GCAEF operation, because of the 1,000 direct QSLs he has answered.

Don VERAJT was very active as VR5AB, but has apparently returned home since he has been suffering from financial problems. The ZMT permit will be valid for one year.

Rhodes Island activity is planned for this winter. The dates are 14/12, 15/12, 16/12. The anticipated frequencies are 14195, 21245 and 28345; listening 5 kc. up. Keep an ear out for Don as host.

Channel 0. RCHT calls from Guernsey in the Channel Islands. To help anybody interested in working this rare country/prefix, Dick has available a list of skeds, l.e. times and frequencies that he will be active on and looking for contacts. The sked list covers the whole year, with skeds from 160 right through to 10 m. If you are interested in obtaining a list, send Dick an a.s.e. and an IRC and he will reply via airmail. Dick's address is: R. Taylor, 10 Cour de Longue, St. Saviour's, Guernsey, Channel Islands.

Skeds for March are: 10th, 14186 a.s.b. at 0730z and 14043 e.s.b. at 1000z, 17th, 21013 e.s.b. at 0730z and 21243 a.s.b. at 0900z. Altogether 141 skeds are listed for March, but the ones listed here are the best for VK. On the average, Dick receives 100 cards per week, but peak weeks have exceeded 200. Therefore, to be sure of receiving a QSL, the following must be observed: Write the month in words, not as a number; use GMT time; and send a frequency with one IRC. (These rules could apply when seeking a reply from any rare DX station. Check at the Post Office to see how many IRCs are needed for an airmail reply, if wanted.)

QSL MANAGERS

- CR6LF—WHINK
- CR7GA—WASHUP
- EPF7D—WASERS
- FPAA—BLAKT
- GP7A—WASHUP
- HSAL—DLTK
- KV4YE—WHINK
- KWA—WHINK
- PIXA—DLTF
- SVOWN—KEUR
- TAIR—DLTK
- TAE—VESAB
- TUAY—DLTF
- VK8J—K8UW
- VK8V—DLTK
- VP1RC—WBEFA
- VP1VR—WAVPD
- VP2RE—WBEFA
- VP3GRN—WAYHB

- VP2GSM—WAYHB
- VP2SAB—W82WOW
- VP2K—WASINK
- VR5AE—VESAB
- VU7AJ—WAKNFC
- XE1PU/XF4—XELJ
- XE2LOW—W82GQK
- ZD8A—W82GQK
- ZD8JL—W82WOW
- JA3CU—DLTF
- JA3D—W82GQK
- JA3M—K2KTX
- SR4S—W82GQK
- SV4AL—DLTK
- SV4G—DLTK
- SV4JL—DLTK
- TP4AR—WABRE
- W82B—W82GQK
- XS5AA—WYRC

SILENT KEY

It is with deep regret that we record the passing of the following Amateurs:

VK5NK (ex VK8NK)—
 Ralph James Knight.

FEDERAL

RESERVATION OF CALL SIGNS

Mr. Carroll, Controller, Radio Branch, P.M.G.'s Dept., during a recent discussion with Federal Executive, pointed out that where a licensee has died, it is policy of the Department not to re-issue his call sign for five years, unless in special circumstances. Where very special circumstances exist, call signs are not re-issued for ten years. In the event of unexpired call signs, these are reserved for two years where no special reasons are given, but consideration will be given to the reservation of call signs for greater periods if, for example, a licensee is transferred interstate or overseas, but intends to return to his original call area.

SPECIAL INTERSTATE CALL SIGNS

We have been informed by the P.M.G.'s Dept. that it has been decided to set aside a block of call letters from which allocation may be made to Amateur licensees who are subject to frequent interstate transfers in their work and desire to retain the basic call letters by which they are known throughout the Amateur fraternity. It will, of course, be necessary for the numeral denoting the particular State to be changed when such transfers are effected and application must be made to the Superintendent in the State in which the station is to be established before removing it to another address, in accordance with the provisions of paragraph 87 of the Amateur Handbook.

Call signs are reserved for use in the various States as follows:—

N.S.W.	VK2CAA - VK2CBZ
Vic.	VK3CCA - VK3CDZ
Qld.	VK4CEA - VK4CFZ
S.A.	VK5CGA - VK5CHZ
W.A.	VK6CIA - VK6CJZ
Tas.	VK7CKA - VK7CJZ

An applicant for a call sign from the above-mentioned series will be required to furnish satisfactory evidence that his employment is likely to result in being transferred interstate at some future date.

The above-mentioned arrangement is being introduced on a trial basis for three years and, of course, will apply to full privilege licence holders only.

RECIPROCAL LICENSING IN FINLAND

We have received from Nilo OH2KK, the Secretary of S.R.A.L., some information sheets about regulations for Amateur Radio in Finland. Any Amateurs intending to travel to Finland can obtain such information from P.E. or write to S.R.A.L., P.O. Box 10306, Helsinki 10, Finland. In short, OH licences will be granted to the citizens of Australia as well as about 12 other countries.

JAMBOREE-ON-THE-AIR

The Boy Scouts World Bureau indicates that the 12th Jamboree-on-the-Air will be held in the third week in October, 1969, making the date for 1969 as 18th-19th, October. National organisers of J.O.T.A. may be interested to contact L. Jarrett, of the World Bureau, on the 10 and 12 metre bands most week-end using his HB9BMS call sign.

VICTORIAN DIVISION STATE CONVENTION

will be held on
 15th and 16th MARCH

at
 BENDIGO

Convention Dinner, Sunday Lunch
 and Afternoon Tea, \$4.50, or
 Sunday activities only, \$2.

Talk-in facilities on Channel A FM.
 Trade Displays, Competitions, and
 Entertainment.

Reservations to be made with Bill Sadler,
 VK3AMZ, 304 Melvor St., Bendigo, Vic.,
 3550, no later than 7th March, enclosing
 \$2 per head deposit.

TOWNSVILLE

Amateur Radio Club

The 1969 Class for those inter-
 ested in obtaining an Ama-
 teur Licence begins on:

Saturday, 8th March, 1969.

Time: 8.30 a.m.
 Location: 4TO Auditorium.

Class Instructor: L. Nosedá,
 VK4EX.

For further information contact:
 P. J. Lindsay, VK4ZPL/T, Tel. 6161

FREE QSL SAMPLES

and Stationery with
 Australian Designs

KARL KHUEN-RYK

16 COWRIE CRES., MT. PLEASANT,
 W.A., 6153

REPAIRS TO RECEIVERS, TRANSMITTERS

Constructing and testing: xtal conv.,
 any frequency; OS-ers, R9-ers, and
 transistorised equipment.

ECCELESTON ELECTRONICS

146a Cotham Rd., Kew, Vic. Ph. 80-3777

Stockists of Radio and Electronic Components for the Amateur Constructor and Hobbyist

First Ring, Write or Call on

WILLIAM WILLIS & Co. Pty. Ltd.
 430 Elizabeth St., Melbourne. Ph. 34-6539

HAMADS

Minimum \$1 for forty words.

Extra words, 3 cents each.

HAMADS WILL NOT BE PURCHASED UNLESS
 ACCOMPANIED BY REMITTANCE.

Advertisements under this heading will be accepted only from Amateurs and S.W.I.s. The Publishers reserve the right to reject any advertising which, in their opinion, is of a commercial nature. Copy must be received at P.O. 36, East Melbourne, Vic., 3002, by 8th of the month and remittance must accompany the advertisement.

AIKI 707 professional deluxe, hi-fi Tape Recorder and reproducer, in as new condition. Dual track, single lever speed change mechanism, automatic shut off, loudspeaker, tape index counter, large VU meter. Can be used for making recordings of excellent quality from mic. or extended program sources, AM/FM radio tuners, record players, TV sets, etc. May be used in either vertical or horizontal position. Complete with dynamic mic. in, spool, service tables, instruction book. Spins 30 to 12000 c.p.m. at 7.5 in./sec. plus or minus 3 c.p.m. S/N ratio more than 50 db. Dual track record play and erase heads, max. reel size 7 in. Output power 5 watts max. power requirements 100/230V, 50 or 60 c.y. \$140. A. Swinton, Kulnura, N.S.W., 2251. Phone 261.

FOR SALE: Apache Tx, five-band with S8-10 S.A.B. Adaptor, excellent condition, \$200. BC34S Receiver, 1000 and 5000 cycles, 1000 and 5000 Hz. Phone 86-4035 (home), 02-6025 (bus.) (Melbourne).

FOR SALE: Collins 302C-3 RF Wattmeter. Switch for forward and reflected power. Dual scale, 300 watts and 2000 watts, very accurate, as new. \$95. A. Swinton, Kulnura, N.S.W. VK2AAK.

FOR SALE: FL100C Transmitter, five-bands, excellent condition, \$225. Also Star SR900 Receiver, double conversion on 80 metres, triple conversion on other bands, pre-selector, 1st local oscillator xtal controlled, beautiful condition, twelve band positions, \$240. VK3CH, A. Nunn, 10 Arcady Gr., Vermont, Vic., 3133.

FOR SALE: Galaxy V. (less power supply), Galaxy Remote VFO, Heath SR200 Linear, \$675. R. Miradas, Box 1277, Canberra City. Phone 48-2663 (days).

FOR SALE: Hi-Gain 2048A 4-element 20 metre beam. New, still in box, \$140. R. Miradas, Box 1277, Canberra City.

FOR SALE: Model 3233 Collins Transmitter, latest model, 100 w. output, as new. A. highly flexible transmitter, 3.4 to 29.7 Mc., p.p.s. 175 w. input, 100 w. output. Grid blocked keying with

adjustable soft or hard output, usable for RTTY. Dual conversion, Collins ALC and inverse feedback. CW spotting control allows zero beating with incoming signal. Fitted with Collins neobeamer filter, bandswitch, etc. 11 selectable crystal positions in 200 Kc. segments. Very high stability, 100 c.y. after warm-up, easy access. Front panel selector provides optional transceiver, CW sidetone for monitoring in receiver, in all, a very high quality transmitter. \$650. A. Swinton, Kulnura, N.S.W., VK2AAK.

FOR SALE: Model 625-1 Collins Transverter for use on 2 and 6 metres by merely pressing a switch to change frequency. In-band, 100 w. supply. 1600w. p.e. 4X150 final on VHF. Any mode of operation—SSB, AM, CW and RTTY, as determined by exciter. Ultimate in frequency stability, 23 switchable crystals, 0.05%, 230 increments 142.5 to 148 Mc. and 49.5-54.2 Mc. Power output 65w. p.p.s. \$680. A. Swinton, Kulnura, N.S.W., VK2AAK.

FOR SALE: Webster Band-Spinner wh. Like new, \$35. R. Miradas, Box 1277, Canberra City.

KW77 Triple Superhet. Amateur Bands Rx, 1.8-29.7 Mc. in seven broadband bands. CW, AM, SSB, xtal cal. fast/slow AGC, \$200 or near offer. R. Collins, VK5RY, 5 Dean Court, Modbury, S.A., 5062. Tel. 64-1210.

SELL: Edgystone EC10 fully transistorised s.s.b. and a.m. Communications Receiver. Brand new in original carton with instruction manual. \$175. Roth Jones, Albert Road, Melbourne, Vic., 3004. Phone 26-6911.

SELL: SR820 with spare set of valves, \$180. Drake TR3 Transceiver with remote VFO, power supply, plus spare set of output valves, \$550. SBE3A Transceiver, operates 240v. a.c. or 12v. d.c., microphone and cables, spare set valves and transistors, \$350. H. Wilson, 31 Glenview St., Greenwich, N.S.W., 2055. Telephone 43-2427.

SELL: 400W, 3-band Linear, g.g. 811As, a.c. p.s.u., \$65. 150 mX Transceiver, 150 w. s.s.b. seg. 100 w. p.p.s., \$25. Channel A FM Base Station, A.W.A., 40w. a.c. p.s.u., control unit, \$45. MR10A, Channel A, 30 w. s.s.b. mobile installation, \$50. VK3AST, Phone 787-2318.

WANTED: Johnson Matchbox or Millen Transmatch. Must be in excellent condition. Ph. 86-3321 Ext. 388 (business), 878-4930 (private). P.O. Box 69, Kew, Vic., 3101.

WANTED TO BUY: General coverage Communications Receiver, ART or similar. Condition and price to P. W. Curran, Kilmory P.O., Vic., 3948.

WANTED: Traps 10M and 15M for Hy-Gain TH4 Tri-Band Beam. Replacements for damaged units. Any type, no matter how old. Also want RF1008, SX122, SX117, SX100, or similar. Paul Roduloff, 21 Derby St., Hawthorne, Qld., 4171.

DURALUMIN, ALUMINIUM ALLOY TUBING

IDEAL FOR BEAM AERIALS AND T.V.

★ LIGHT ★ STRONG ★ NON-CORROSIVE

STOCKS NOW AVAILABLE FOR IMMEDIATE DELIVERY

ALL DIAMETERS— $\frac{1}{4}$ " TO 3"

Price List on Request

STOCKISTS OF SHEETS—ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS PTY. LTD.

SALMON STREET,
PORT MELBOURNE, VIC.

Phone: 64-3351 (10 lines)
Telegrams: "Metals," Melb.



HANSON ROAD,
WINGFIELD, S.A.

Phone: 45-6021 (4 lines)
Telegrams: "Metals," Adel.

CALL BOOK

1968-69 EDITION

NOW AVAILABLE!

75 Cents, from your usual Supplier

BRIGHT STAR CRYSTALS

FOR ACCURACY, STABILITY, ACTIVITY
AND OUTPUT



Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE
AVAILABLE IN FT243 HOLDERS:

6280, 4095, 4535, 2760, 2524 Kc.
5,500 Kc. T.V. Sweep Generator Crystals, \$7.25;
100 Kc. and 1000 Kc. Frequency Standard, \$17;
plus Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, \$13 each plus Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 Mc. AND 7 Mc. BAND.

Commercial—0.02% \$7.25, 0.01% \$7.55, plus Sales Tax.

Amateur—from \$6 each, plus Sales Tax.

Regrinds—Amateur \$3, Commercial \$3.75.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carell, Box 2102, Auckland.
Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

LOT 6, EILEEN ROAD, CLAYTON, VIC.

Phone 546-5076

With the co-operation of our overseas associates our crystal
manufacturing methods are the latest.



**VHF
COMMUNICATIONS**

A PUBLICATION FOR THE RADIO AMATEUR
(ESPECIALLY COVERING VHF, UHF AND MICROWAVES)

VHF COMMUNICATIONS, the International Edition, printed in English, of the well established German Publication UKW-BERICHTE, is an Amateur Radio magazine catering especially for the VHF, UHF and Microwave enthusiast.

VHF COMMUNICATIONS will follow the same path as UKW-BERICHTE, by specialising in the publication of exact and extensive assembly instructions for VHF, UHF and Microwave transmitters, receivers, converters, transceivers, antennas, measuring equipment and accessories, which can be easily duplicated. The latest advances in semiconductors, printed circuits and electronic technology are described in great detail. For most articles, all the special components required for the assembly of the described equipment, such as epoxy printed circuit boards, trimmers, coil formers, as well as metal parts and complete kits will be available from the Australasian Representative.

VHF COMMUNICATIONS also features information regarding the development of electronic equipment, measuring methods, as well as technical reports covering new techniques, new components and new equipment for the Amateur.

VHF COMMUNICATIONS is a quarterly, published in February, May, August and November. Each edition contains roughly sixty pages of technical information and articles.

VHF COMMUNICATIONS' subscription rate (air mailed direct from the publisher) is \$5.50 per year. Every copy is dispatched in a sealed envelope to ensure that it arrives in perfect condition.

Some copies of the German edition UKW Berichte are available free for perusal. Subscriptions, either cheque or money order/postal note should be forwarded to the Australasian Representative, Mr. Gordon Clarke, 2 Beaconview St., Balgowlah, N.S.W., 2093, Australia.



**UKW
BERICHTE**

ZEITSCHRIFT FÜR DEN VHF-UHF-AMATEUR
ULTRAKURZWELEN- UND DEZIMETERWELLENTÉCHNIK



... Going SSB?

BAIL ELECTRONIC SERVICES have the answers!
Widest choice from the YAESU Australian Agents.

FRDX-400 Receiver: 160-10 mx, I.F. "T" notch filter, 100/25 Kc. calibrator, selectable slow/fast AGC, provision for internal installation of FET VHF converters, FM with squelch. Laboratory proven, outstanding sensitivity. Can be linked with FLDX-400 for transceiving.

FLDX-400 Transmitter: PA 2 x 6JS6A, 300w. speech peak input. Mechanical filter, VOX, ALC; adaptable to FSK for RTTY.

FTDX-400 Transceiver: 80/10 mx, 400-500w., built-in AC power supply, VOX, ALC, off-set tuning, calibrator . . . the lot!


Also available: Transceiver FT-50, Transmitter FL-50, Receiver FR-50, Low Pass Filter FF-30DX, Type "F" SSB Generator Assembly, SWR Meter K-109, Yaesu valves and spares, Co-ax. Connectors, Hy-Gain (U.S.A.) Beams.

BAIL POLICY: Manufacturer-backed 90-day warranty. All sets are tested before despatch. After-sales service and spares availability.

Full details from the authorised Australian Agent:

BAIL ELECTRONIC SERVICES, 60 Shannon St., Box Hill North, Vic., 3129. Ph. 89-2213

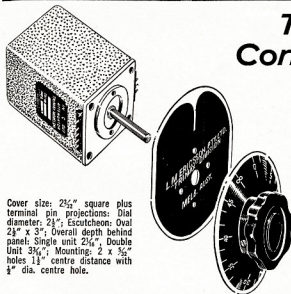Rep. in N.S.W.: A. J. ("SANDY") BRUCESMITH, 47 Hyman Street, Tamworth, N.S.W., 2340. Telephone (STD 067) 66-1010



Cover size: $2\frac{3}{4}$ " square plus terminal pin projections: Dial diameter: $2\frac{1}{2}$ "; Escutcheon: Oval $2\frac{1}{2}$ " x 3"; Overall depth behind panel: Single unit $2\frac{1}{4}$ ", Double Unit $3\frac{1}{4}$ "; Mounting: 2 x $\frac{3}{16}$ " holes $1\frac{1}{2}$ " centre distance with $\frac{1}{8}$ " dia. centre hole.

The Ultimate in Control Reliability!

ATTENUATORS AND FADERS by TRIMAX

The 'Trimax' Model G45 Fader is a new design evolved from experience gained over twenty years of this type of manufacture, and features solid non-staining silver alloy contacts, floating rotor with three contact pressure points, optimum, permanently maintained contact pressure, rigid four pillar construction. Porous bronze main bearing, stainless steel spindle, high quality phenolic resin stud plates with acetal resin rotor bosses, diamond lapped contact surfaces, positive knob stop in addition to individual rotor stop, high stability resistors.



L M ERICSSON PTY. LTD.
"TRIMAX" DIVISION

FACTORY: CNR, WILLIAMS RD. & CHARLES ST., NORTH COBURG, VICTORIA. 'PHONE: 35-1202 . . . TELEGRAPHIC ADDRESS: "TRIMAX" MELB.





TRIO

SSB transceiver

200 watts PEP—7 Bands—A M & C W
and
Power Supply and Speaker Unit



SPECIFICATIONS:

Frequency:	80m Band	3.5-4.0 MHz
	40m Band	7.0-7.5 MHz
	20m Band	14.0-14.6 MHz
	15m Band	21.0-21.6 MHz
	10m A Band	28.0-28.6 MHz
	10m B Band	28.5-29.1 MHz
	10m C Band	29.1-29.7 MHz

Communication Method: SSB (A3J)
AM (A 3H)
CW (A1)

Maximum Input Power: (Xmitter final stage)
200W (PEP)

Standard Input Power: (Xmitter final stage)
180W (PEP) 120W on 28 MHz band only

Antenna Input Impedance: 50-75 ohm

Carrier Suppression Ratio: More than 40 dB

Single Side Band Ratio: More than 40 dB

Mic. Input Impedance: High impedance
(dynamic or crystal mic. recommended)

Xmitter Audio Frequency Characteristics:
300-3,000 Hz (-6 dB)

Receiver Sensitivity: 1 μ V S/N 10 dB
(14 MHz)

Receiver Selectivity: 2.7 kHz (-6 dB)
5.0 kHz (-55 dB)

Spurious Rejection Ratio: More than 45 dB

Image Ratio: More than 60 dB

Undistorted Power Output: More than 1W

Receiver Output Impedance:
SP 500 ohm
PHONE 8 ohm

Power Consumption (using PS-500AC):
450W (At maximum power output)
250W (Receiving Mode)

Tubes and Transistors used:
17 TUBES, 3 TRANSISTORS, 15 DIODES

Dimensions: W: 13 1/4"; H: 8 1/2"; D: 11 1/2"
Weight: 17.6 lb

FOR/FOA SYDNEY: TS 500, \$491.00; PS 500 AC, \$98.00

CONSULT YOUR LOCAL RADIO DEALER, OR

MAIL THIS COUPON *today*

Please forward free illustrated literature and specifications on Trio equipment.

Name

Address



(A unit of Jacoby Mitchell Holdings Ltd.)
376 EASTERN VALLEY WAY, ROSEVILLE, N.S.W.
Cables and Telegraphic Address: 'WESTELEC',
Sydney. Phone: 40 1212

LOW DRIFT CRYSTALS



1.6 Mc. to 10 Mc.,
0.005% Tolerance, \$5



10 Mc. to 18 Mc.,
0.005% Tolerance, \$6



Regrinds \$3

THESE PRICES ARE SUBJECT
TO SALES TAX

SPECIAL CRYSTALS:
PRICES
ON APPLICATION

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY,
VIC., 3126

Phone 83-5090

LOG BOOK

IS NOW AVAILABLE

Larger, spiral-bound pages
with more writing space.

Price 75c each

plus 17 Cents Post and Wrapping

Obtainable from your Divisional
Secretary, or W.I.A., P.O. Box 36,
East Melbourne, Vic., 3002

TRIO TR2E 2 METRE TRANSCEIVER

- Triple conversion receiver with crystal locked 2nd and 3rd oscillators for maximum selectivity and sensitivity.
- Separate VFO tuning for both receiver and transmitter.
- Nuviator RF amplifier.
- Provision for crystal locking of the transmitter.
- 12 volts DC (internal transistor power supply) and 230/240 volts AC operation.
- Noise limiter and squelch.
- 17 tubes, 4 transistors and 7 diodes.
- 1 microvolt sensitivity for 10 db. S/N ratio at 146 Mc.
- "S" meter, RF output meter, and "netting" control.

Price: \$282.00

MILLER 8903B PRE-WIRED I.F. STRIPS

455 Kc. centre frequency, 55 db. gain, uses two PNP transistors and diode detector. Bandwidth 5 Kc. at 6 db. DC requirements: 6 volts at 2 mA.

Price: \$9.70

Plus pack and post 25 cents

VALVE SPECIALS

ATS25 ceramic base 807, 70c or three for \$2.

815, 70c.

6AC7, 20c or 12 for \$2.

6J6, 30c or 7 for \$2.

6CQ6, 20c or 6 for \$1.

VR150/30, 75c or 3 for \$2.

QB2/250 (813), new and boxed, \$7 ea.

6H6 metal, 20c each.

DM71 indicator tube, 40c ea. or 6 for \$2.

6F33, 30c ea.

RESISTORS

Mixed Values

\$2 per 100

plus postage 20 cents

CAPACITORS

Mixed Values

80 for \$2

plus postage 20 cents

STAR ST-700 TRANSMITTER

SSB — AM — CW

80 Metres to 10 Metres

- Ultra-precision three-stage double gear tuning mechanism, completely free of backlash, spreads each 600 Kc. over 1.68 metres with 1 Kc. dial calibration.
- Stability better than 100 cycles. "Vackar" type VFO. Voltage regulated power supply.
- Uses mechanical filter at 455 Kc. specially designed for SSB. Selectable upper or lower sideband. Carrier and sideband suppression 50 db. or more.
- May be connected with STAR SR-700A receiver for transceive operation.
- Fully adjustable VOX and ANTITRIP circuits for automatic transmission/reception.
- Press-to-talk relay, break-in keying and sidetone oscillator for CW monitoring.
- Automatic level control circuit assures high quality distortion free SSB.
- Built-in antenna relay.
- Final stage uses two 6146s in parallel with conservatively rated input of 250 watts PEP on SSB and CW, 100 watts on AM.
- Built-in heavy duty power supply with adequate reserve margin assures trouble-free operation.
- Power supply 220 to 240 volts AC 50 cycles.

Price: \$519.50

CARBON POTS

20 cents ea.

WIRE-WOUND POTS

40 cents ea.

3000 TYPE RELAYS

large range

Only 50 cents ea.

VACUUM SEALED RELAYS

mainly 24 volts

50 cents ea.

TRANSISTORISED COMPUTER BOARDS

from \$3

FULL RANGE OF MULTIMETERS

STAR SR-700A RECEIVER

SSB — AM — CW

- Ultra-precision three-stage double gear tuning mechanism, completely free of backlash, spreads each 600 Kc. over 1.68 metres with 1 Kc. dial calibration.
- Stability better than 100 cycles. "Vackar" type VFO. Voltage regulated power supply.
- Triple conversion. IF's 1650 Kc. and 55 Kc. First and third oscillators crystal controlled.
- Imagine ratio better than 60 db. on all bands. Beat interference below noise level.
- Variable selectivity band pass filter at 55 Kc. provides steep cut offs and a good shape factor. Four positions: 0.5, 1.2, 2.5 and 4 Kc. (at 6 db. down).
- T-notch filter provides better than 50 db. attenuation.
- Variable decay AGC. Variable BFO tuning.
- Output terminal on VFO for transceive operation.
- Product detector for SSB/CW. Diode detector for AM.
- Noise limiter with adjustable clipping level operates on AM, SSB and CW.
- Built-in 100 Kc. crystal calibrator (crystal included). Zero adjustment on VFO.
- Sensitivity better than 0.5 μ V. for 10 db. S + N ratio on SSB and CW, better than 1 μ V. on AM.
- Power output, 1 watt. Impedance, 4 ohms.
- 13 tubes, 6 diodes.

Price: \$461.50

MARCONI TF885A VIDEO OSCILLATOR

Price: \$120

SANSEI SE405 S.W.R. BRIDGE

1 Mc. to 150 Mc., also doubles as a Field Strength Meter

Price: \$21 inc. tax

WE SPECIALISE IN CRO's

Cossor, Solarton, Dumont, A.W.A., Philips, E.M.I.

From \$80

See us for all Marconi Test Equipment

All Prices Subject to Alteration without Notice. All Items Freight Extra.

UNITED TRADE SALES PTY. LTD.

280 LONSDALE ST., MELBOURNE, VIC. (Opp. Myers)

Phone 663-3815


radioparts

PROPRIETARY LIMITED

CUSTOMER SERVICE



NEW ... AC BRIDGE!

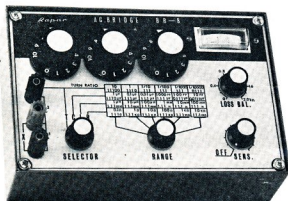

"Rapar" model BR8

Measures:

*Resistance, Capacitance,
Inductance and
Transformer Turns Ratios*

Price: \$46.00 + 15% S.T.

SPECIFICATIONS:

Resistance: 0.1 ohm to 11.1 megohm in 5 ranges

Accuracy: 0.1 ohm to 10 ohm $\pm 2\%$ ± 0.1 ohm

10 ohm to 5 megohm $\pm 1\%$

5 megohm to 11.1 megohm $\pm 5\%$

Inductance: 1 μ H. to 111 H. in five ranges

Accuracy: 1 μ H. to 100 μ H. $\pm 5\%$ ± 1 μ H.

1 mH. to 111 H. $\pm 2\%$

Capacitance: 10 pF. to 1110 μ F.

Accuracy: 10 pF. to 100 pF. $\pm 2\%$ ± 10 pF.

111 pF. to 111 μ F. $\pm 1.5\%$

111 μ F. to 1110 μ F. $\pm 5\%$

Turns Ratio: To 11100 : 1 $\pm 1.5\%$

Bridge Frequency: 1 Kc.

Power Source: 1 x 216 9-volt battery

Size: 7½" wide x 5" high x 3" deep.



RADIO PARTS PTY. LTD.

MELBOURNE'S WHOLESALE HOUSE

562 Spencer St., Melbourne, Vic., 3000. Phone 329-7888, Orders 30-2224

City Depot: 157 Elizabeth Street, Melbourne, Vic., 3000. Phone 67-2699

Southern Depot: 1103 Dandenong Rd., East Malvern, Vic., 3145. Ph. 211-6921

OPEN SATURDAY MORNINGS!